

**NANYANG
TECHNOLOGICAL
UNIVERSITY**
SINGAPORE


MA2012 INTRODUCTION TO MECHATRONICS SYSTEMS DESIGN

Lecture 6

Prof Ang Wei Tech

College of Engineering
School of Mechanical and Aerospace Engineering

Mechatronic System Components

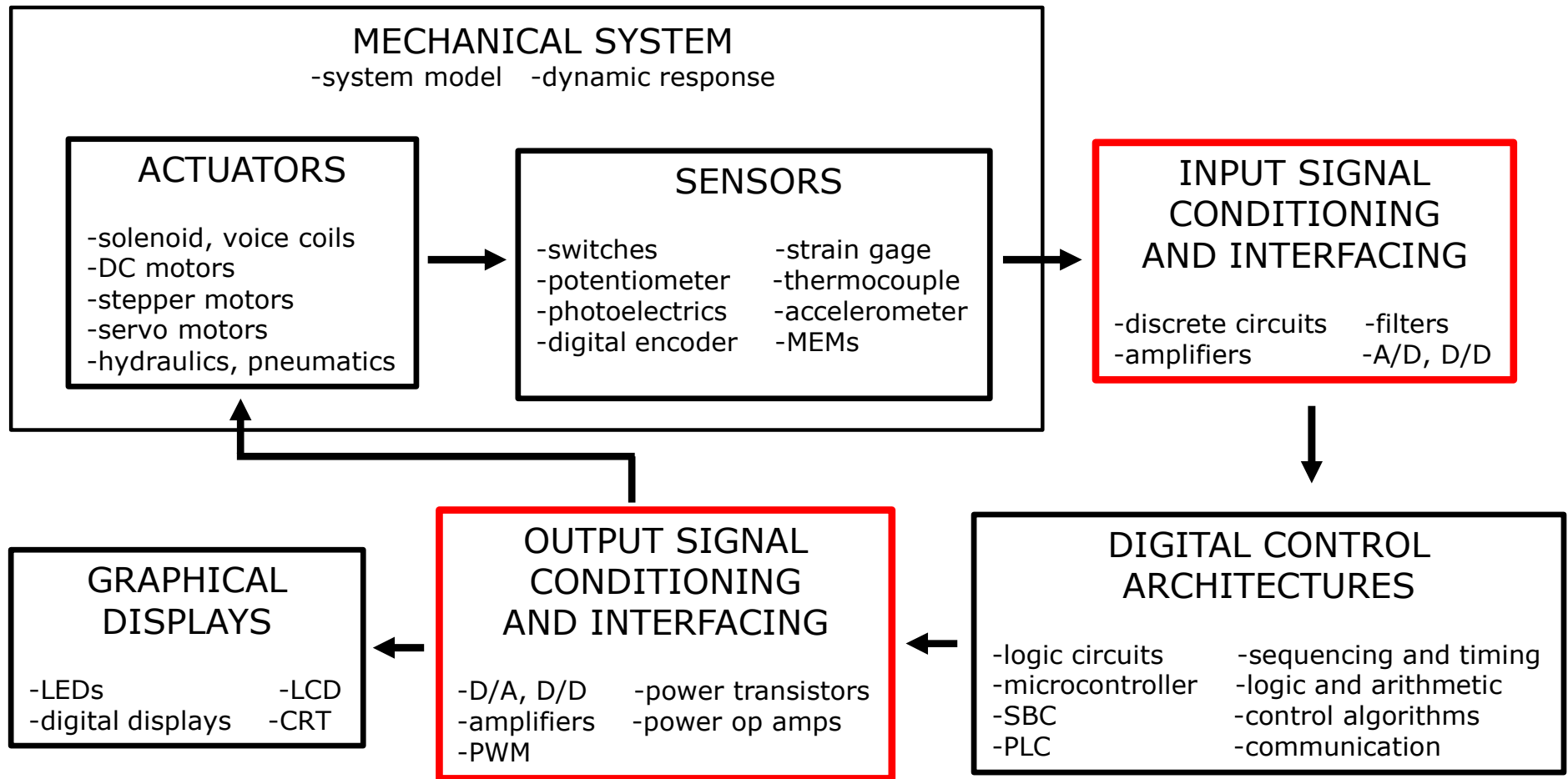

Signal Conditioning

INPUT SIGNAL CONDITIONING

- To convert the output of sensing elements into a form suitable for further processing
- Types
 - Analog-to-Digital conversion
 - To reduce noise level
 - To enhance signal power
 - To improve noise immunisation
 - To eliminate non-linearity

OUTPUT SIGNAL CONDITIONING

- To convert the output of digital control systems (i.e. MCU, PC) into a form suitable for interfacing with output elements
- Types
 - Digital-to-Analog conversion
 - To amplify signal (power, current, voltage, etc.)
 - To improve noise immunisation


Deterministic vs Random Signals

- Deterministic Signals

- Value can be predicted exactly, after the observation period T_0

- Random Signals

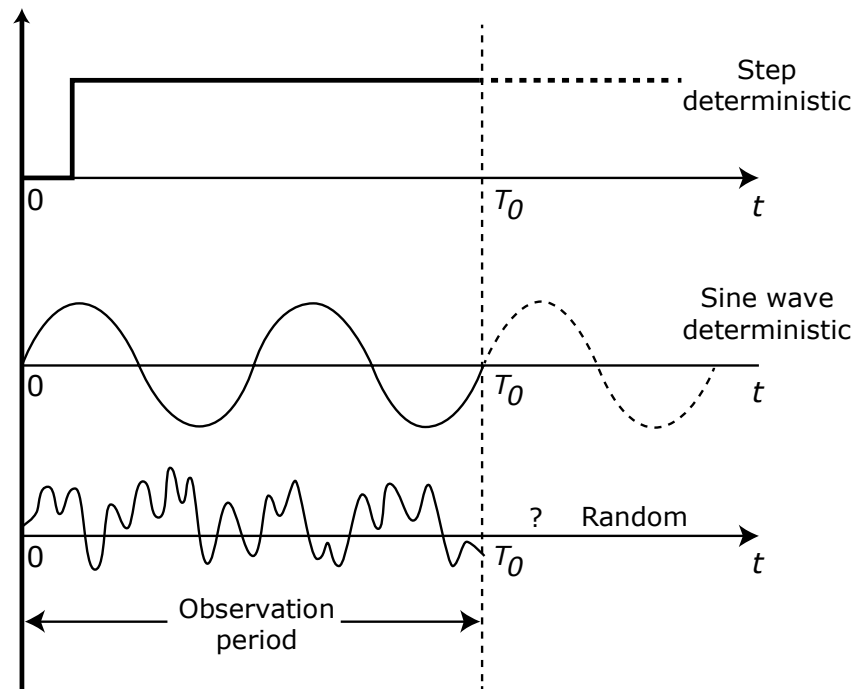- Value cannot be predicted exactly, after the observation period T_0
- The signal cannot be represented by a continuous algebraic equation $y(t)$ for the signal y at time t



Deterministic vs Random Signals

Randomness

- A real process has many parameters that cannot be exactly known, because of the randomness of nature
- Absolutely clean signal does not exist, if resolution is allowed to be infinitesimally small, i.e. Observed randomness is dependent on resolution
- E.g. Leaves falling from a tree



Randomness: leaves falling from a tree


Randomness



- E.g. Leaves falling from a tree:
 - Resolution = $1 \text{ m}^2 \rightarrow$ noisy outcome
 - Resolution = $100 \text{ m}^2 \rightarrow$ clean outcome

Randomness

Click image to play video

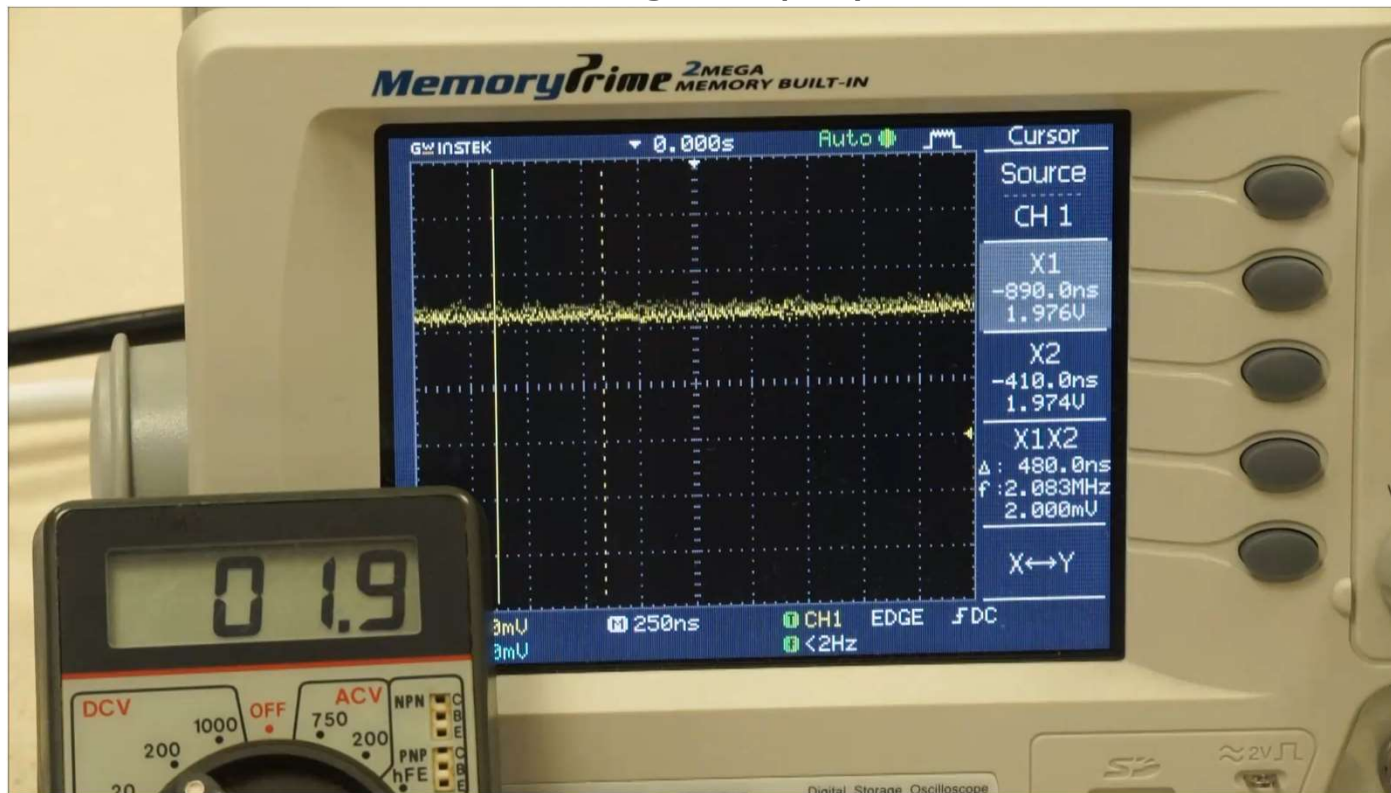


Voltage source

- E.g. A voltage source:
 - Resolution = 0.1 V → clean voltage
 - Resolution = 0.001 V → noisy voltage


Noise

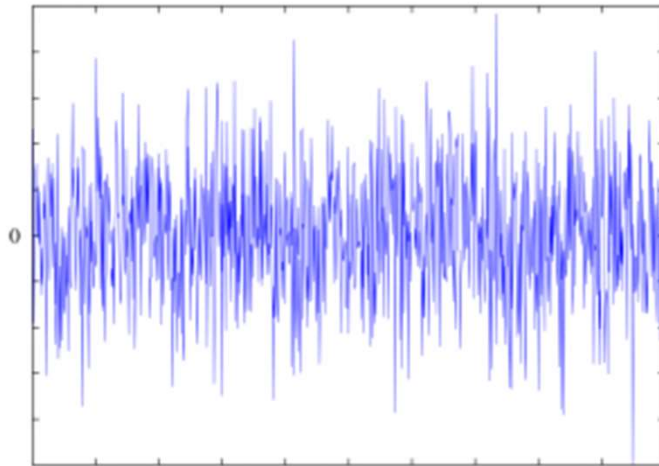- Noise is unwanted signal
- White noise = signal with equal power in all frequencies and zero mean, i.e. totally random signal




White noise

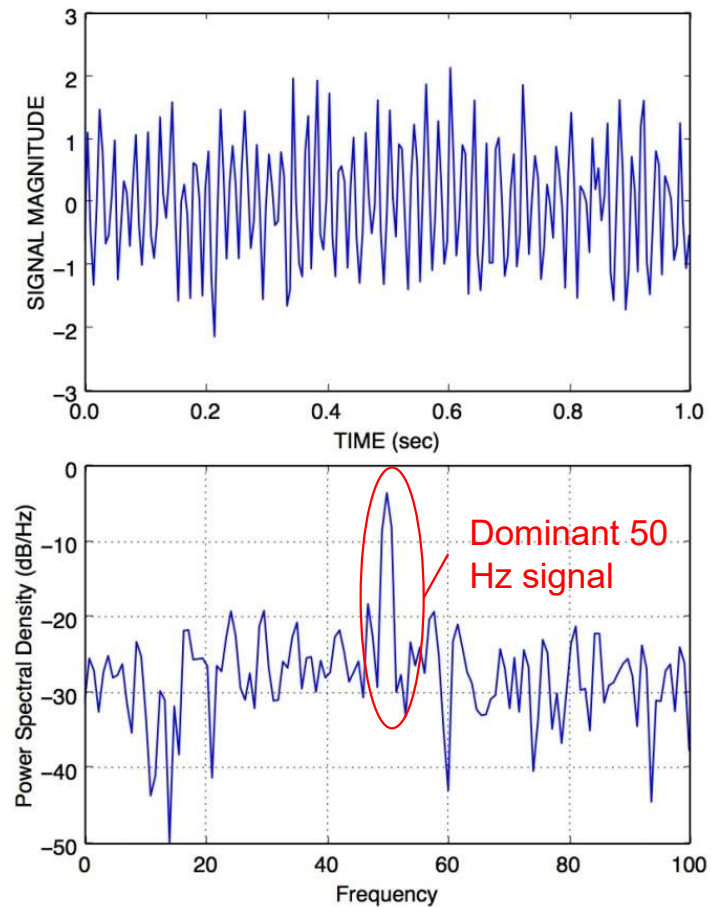- Coloured noise = unwanted signal with certain bias or distinctive frequency(ies)



Coloured noise

Noise

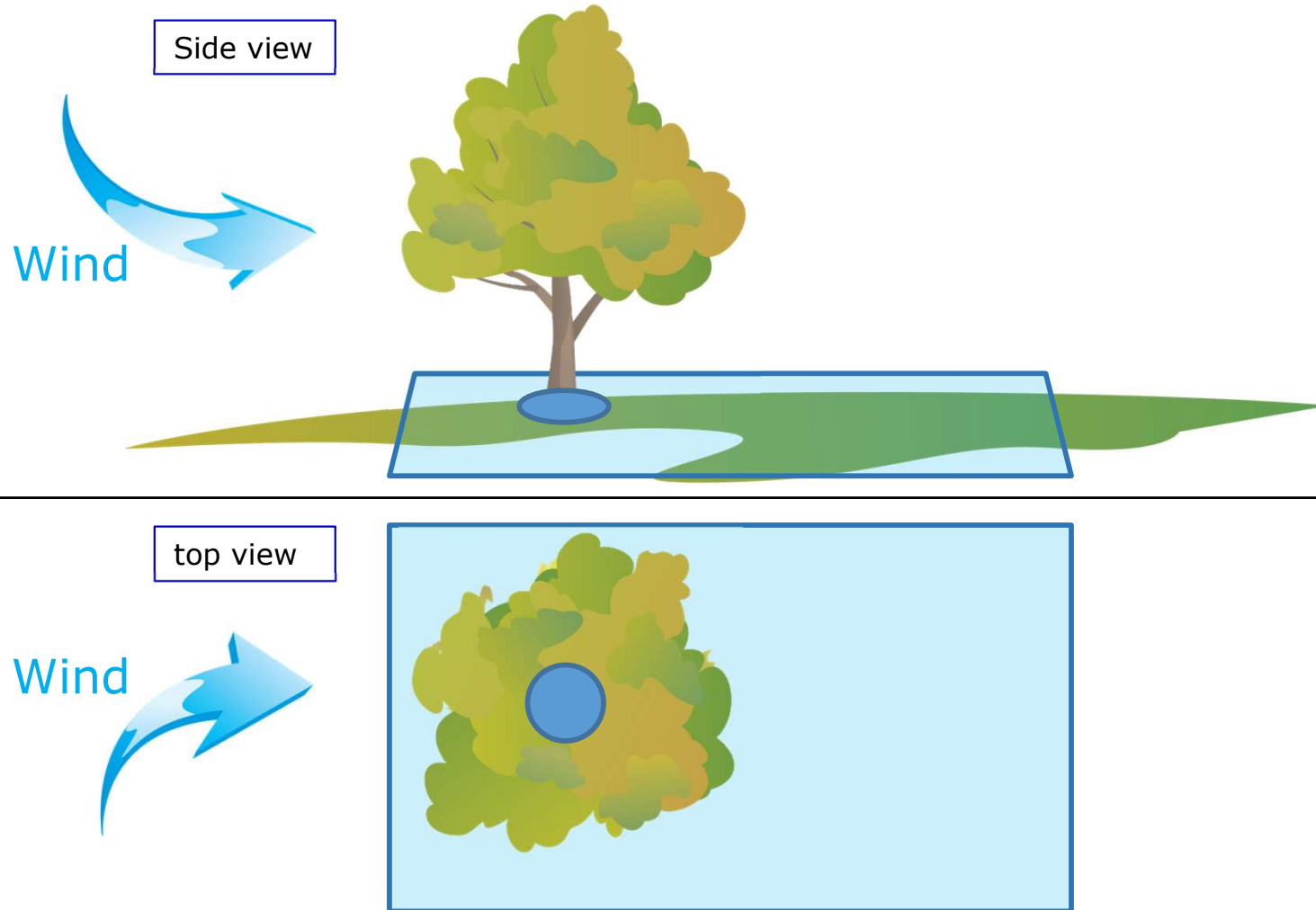

- Coloured Noise e.g. Falling leaves with wind blowing
- Mean of the leaves spread is no longer at the foot of the tree, i.e. non-zero mean or bias

Signal-to-Noise Ratio

- Signal-to-noise ratio is defined as the ratio of the power of a signal (meaningful information) and the power of background noise (unwanted signal):

- $$SNR = \frac{\text{Total Signal Power}}{\text{Total Noise Power}} = \frac{W_S}{W_N}$$

- Expressed in decibel:

- $$SNR = 10 \log_{10} \left(\frac{W_S}{W_N} \right) dB$$

Noise Sources

INTERNAL NOISE SOURCES

- Johnson or thermal noise
 - Random, temperature-induced motion of electrons and other charge carriers in resistors and semiconductors gives rise to a corresponding random voltage
 - White noise proportional to the absolute temperature
- Shot noise
 - Random fluctuations in the rate at which carriers diffuse across a junction of transistor
 - Another source of white noise


Noise Sources

EXTERNAL NOISE AND INTERFERENCE SOURCES

- AC power circuits operating at 220V, 50Hz (US:110V, 60Hz)
 - Produce “mains pick-up” or “hum” which is a corresponding sinusoidal interference signal in the measurement circuit
- Fluorescent lighting arcing at 2x per cycle of the AC power
 - Arcing is the process of raising the potential to cause electrical current to flow between anode & cathode through the inert gases inside the tube
- Radio frequency (RF) interference
 - Transmitters, welding equipment and electric arc furnaces can produce interference at frequencies of several MHz

Input Signal Conditioning Elements

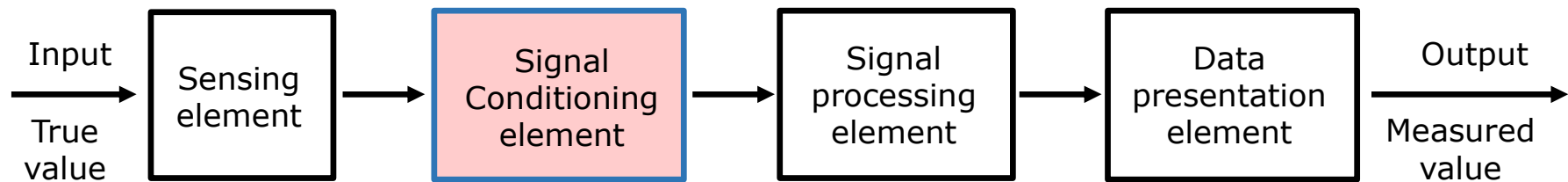- Suitable forms
 - DC voltage [MA 2012]
 - DC current; Variable frequency AC voltage
- Examples:
 - Deflection bridges
 - Operational amplifiers (Op-Amp)
 - Filters





Input signal conditioning elements

Deflection Bridges

- Quarter Bridge

- Voltage output:

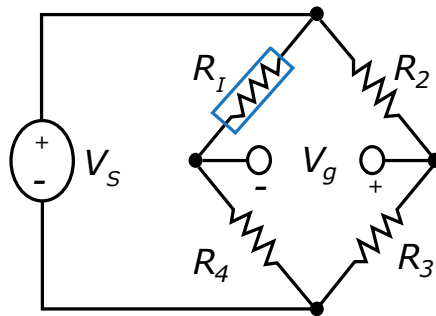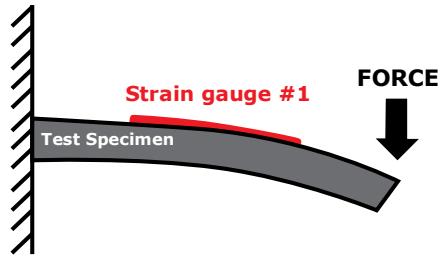
$$V_g = V_S \left(\frac{1}{1+R_4/R_I} - \frac{1}{1+R_3/R_2} \right)$$



Quarter bridge

- Half Bridge


- Double sensitivity over 1/4B

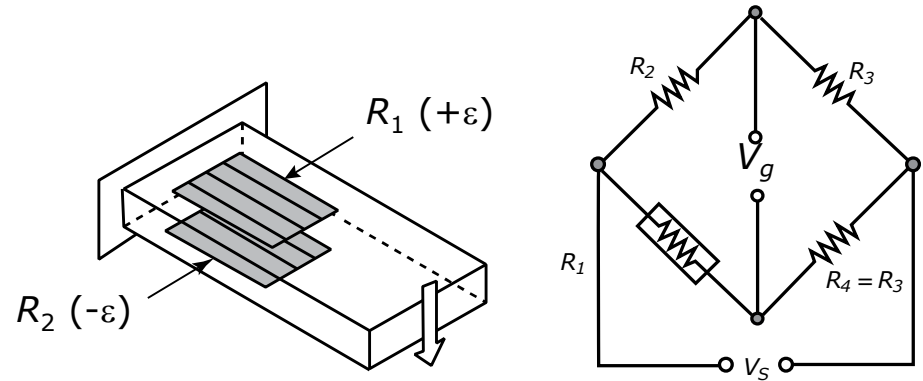

Half bridge

- Full Bridge

- Simplicity & linearity over 1/2B

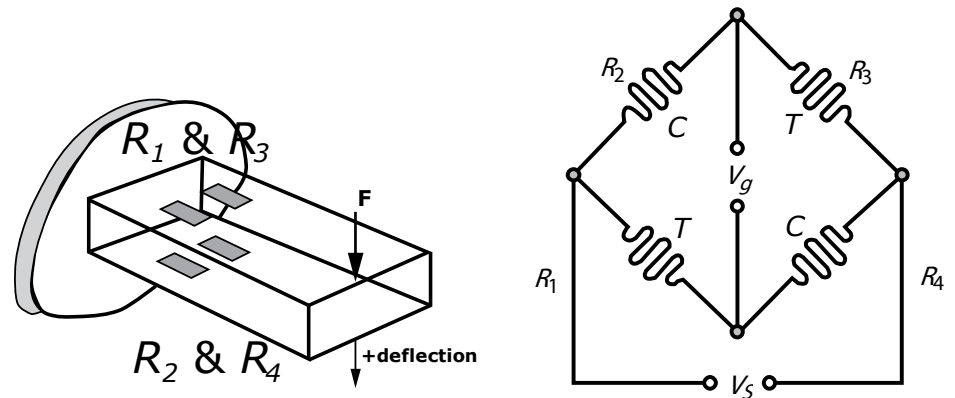

Full bridge


Amplifiers

- The operational amplifiers (op-amps) are used as the basic building blocks for instrumentation and power amplifiers
- Types of op-amp
 - Inverting
 - Non-inverting
 - Voltage follower
 - Voltage adder
 - Differential

Op-Amp

- Inverting amplifier


$$V_{out} = \frac{-R_F V_{IN}}{R_{IN}}$$

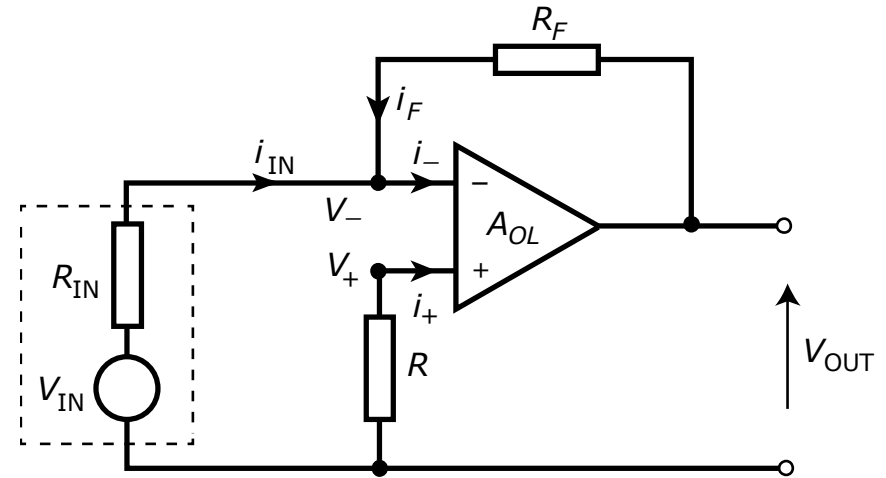

Inverting amplifier

- Non-inverting amplifier
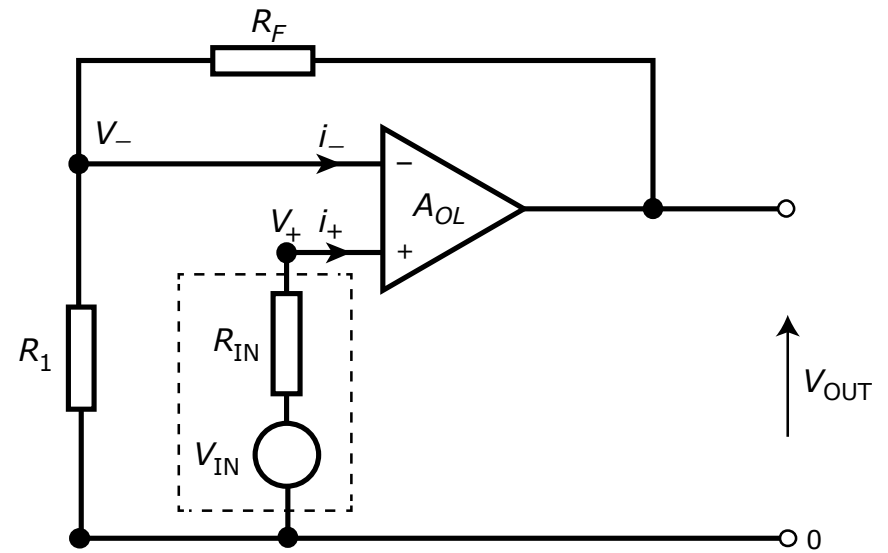
$$V_{out} = \left(1 + \frac{R_F}{R_{IN}}\right) V_{IN}$$




Non-inverting amplifier

Op-Amp

- Voltage follower


$$V_{out} = V_{IN}$$

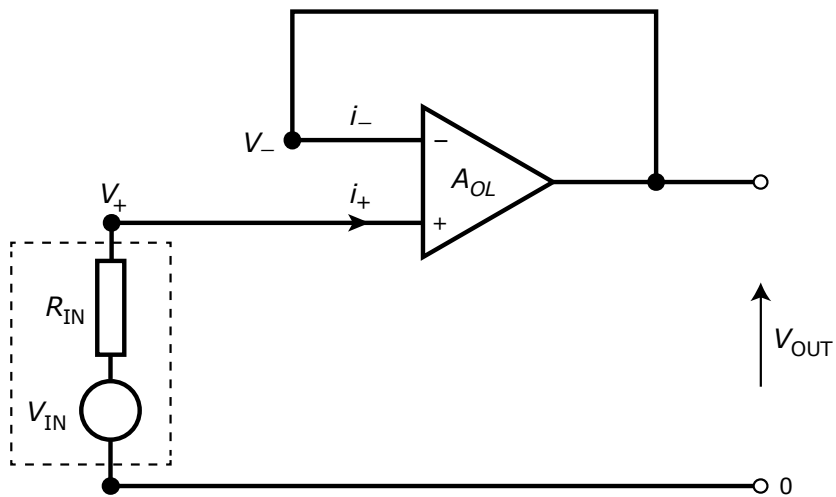

Voltage follower

- Voltage adder
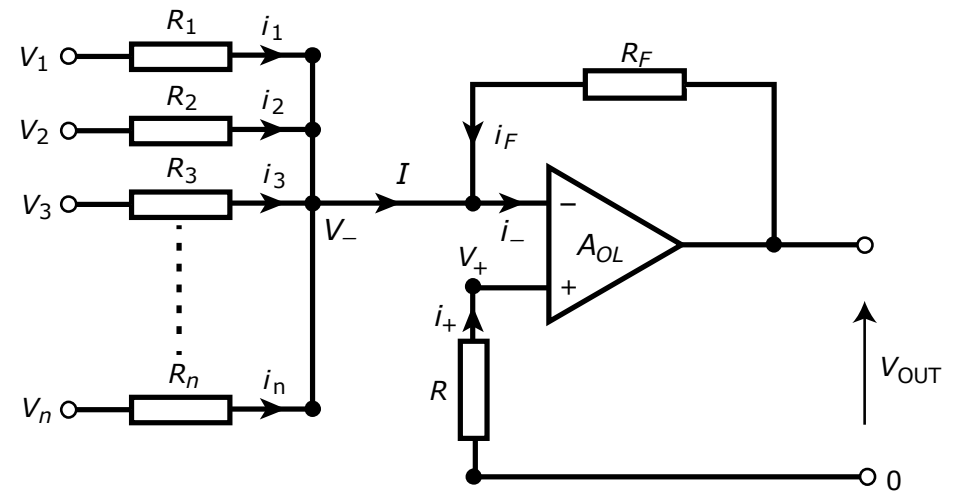
$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$




Voltage adder

Op-Amp


- Differential amplifier
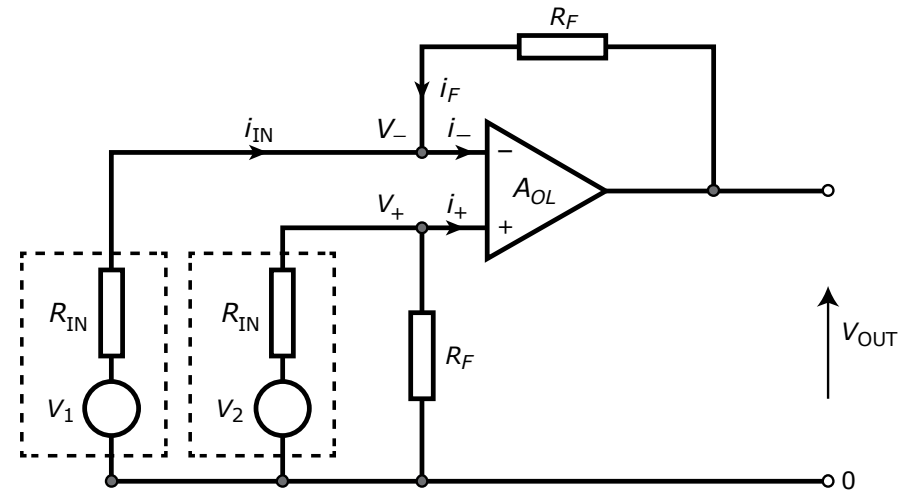
$$V_{out} = \frac{R_F}{R_{IN}} (V_2 - V_1)$$




Differential amplifier

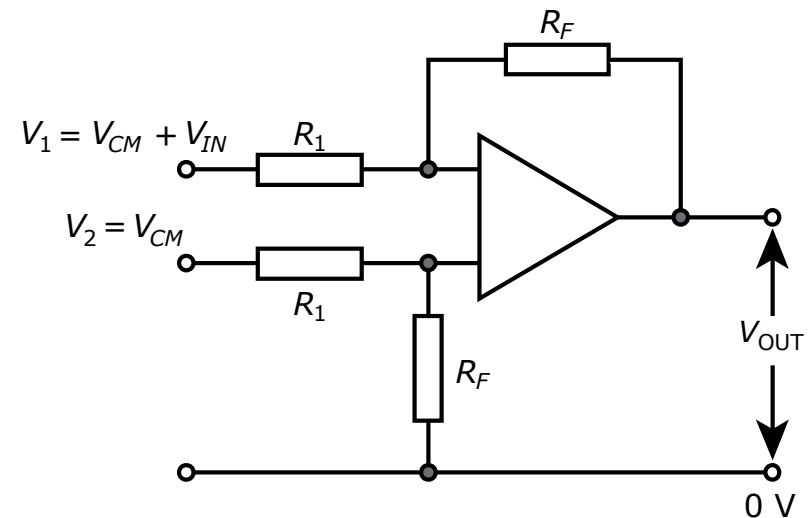- Common mode interference voltages can be successfully rejected




Filtering

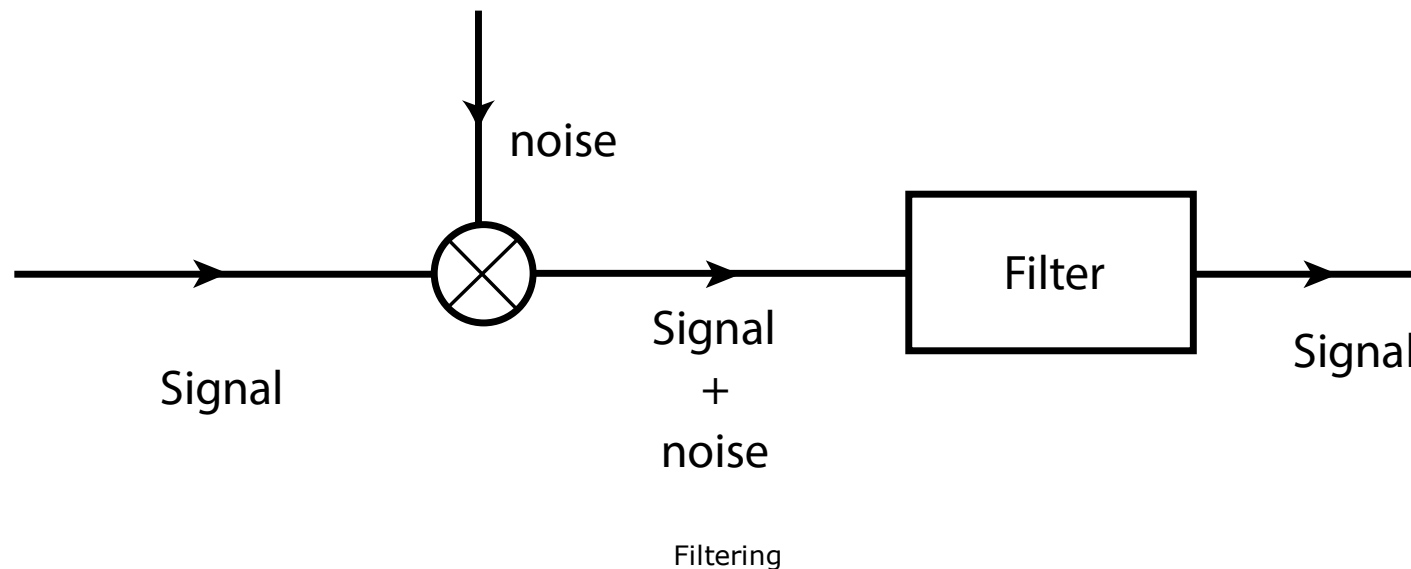- A frequency selective filter is an element which transmits a certain selected range(s) of frequencies and rejects all others
- Analog filter is a network of resistors, capacitors and op amps to process continuous signals
- Digital filter is a computer programmed to process sampled values of a signal




Filtering

- Low & High Pass Filters

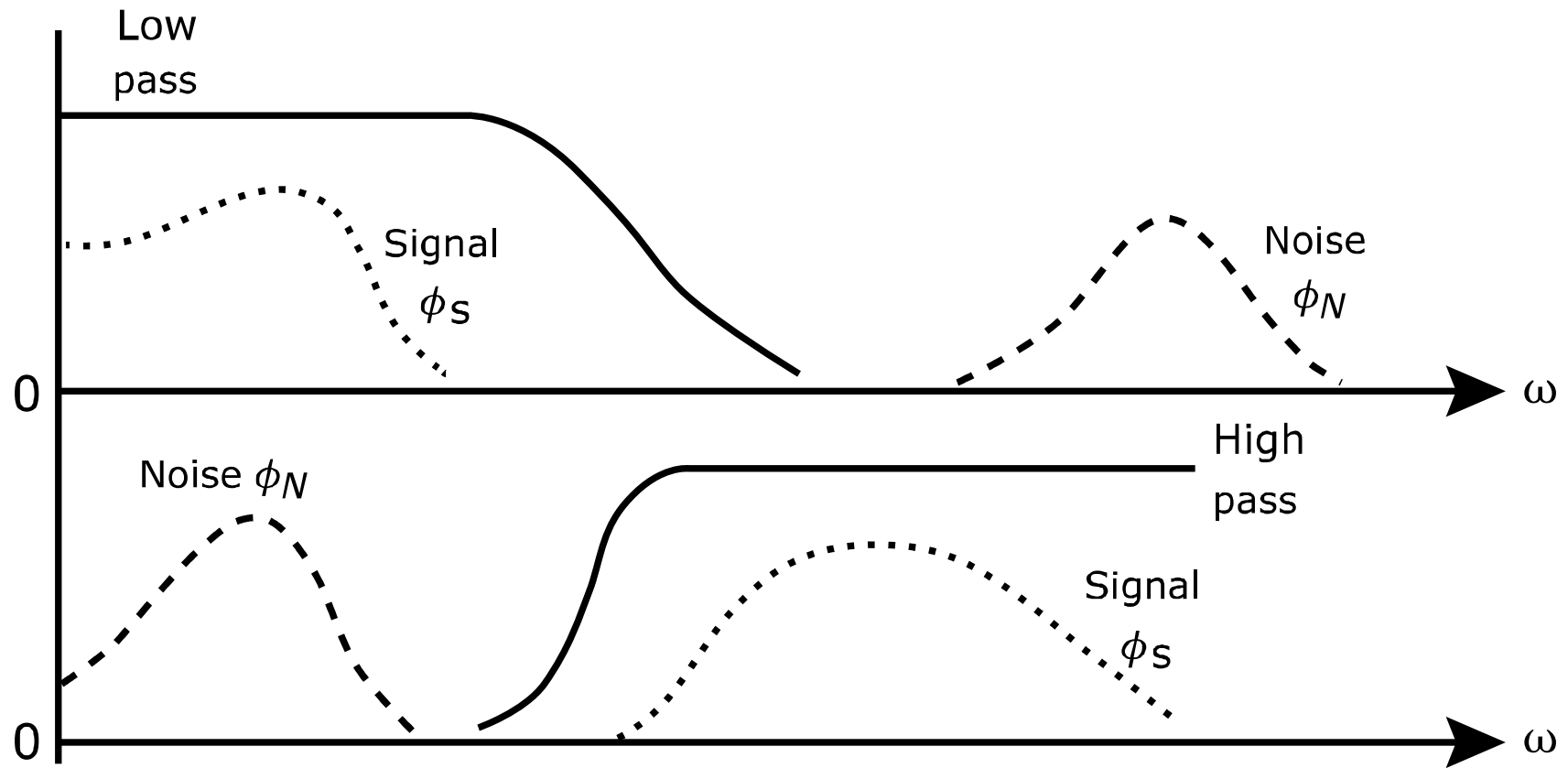


Low and high pass filters

Filtering

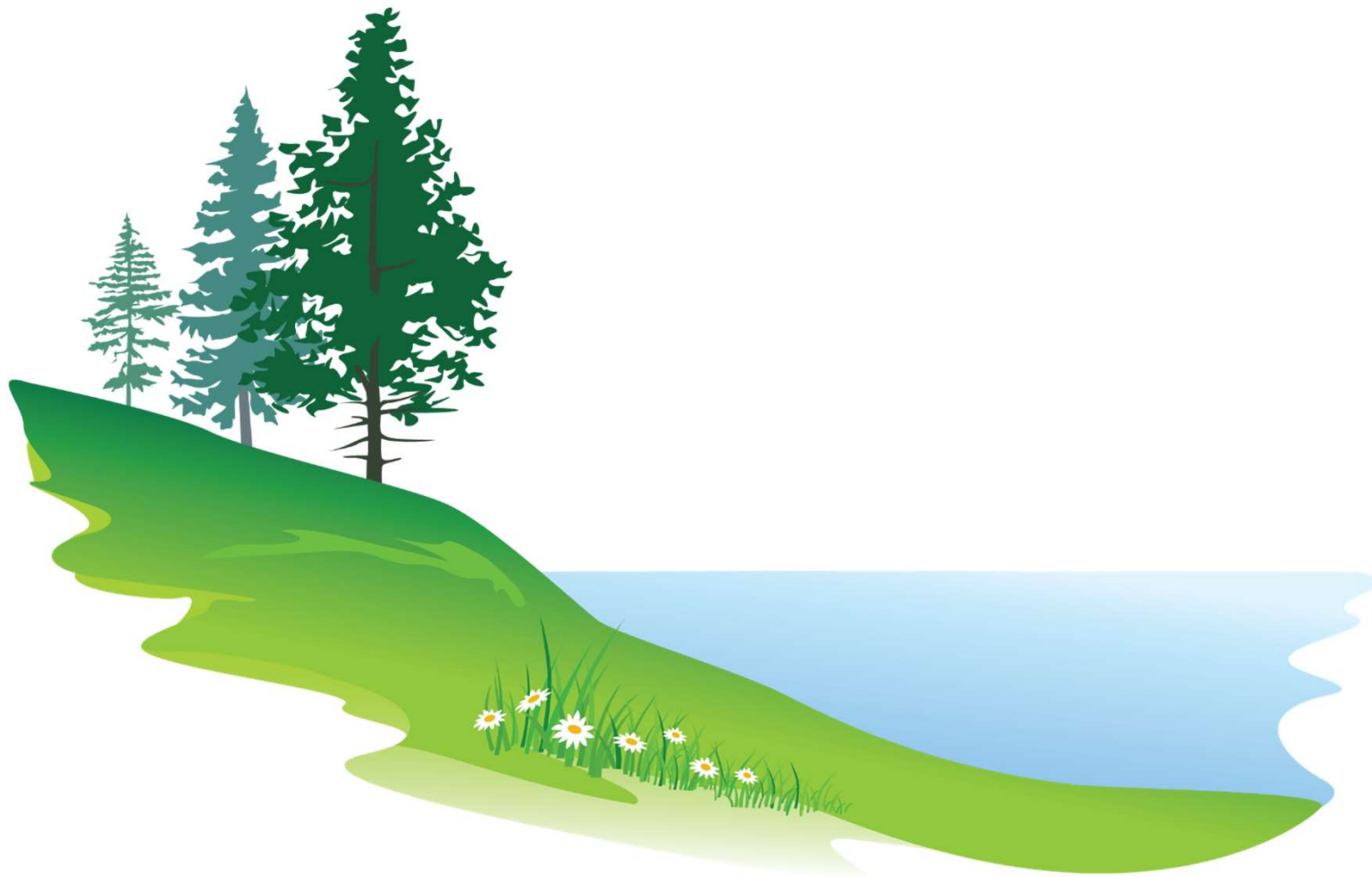

River Stream

Filtering

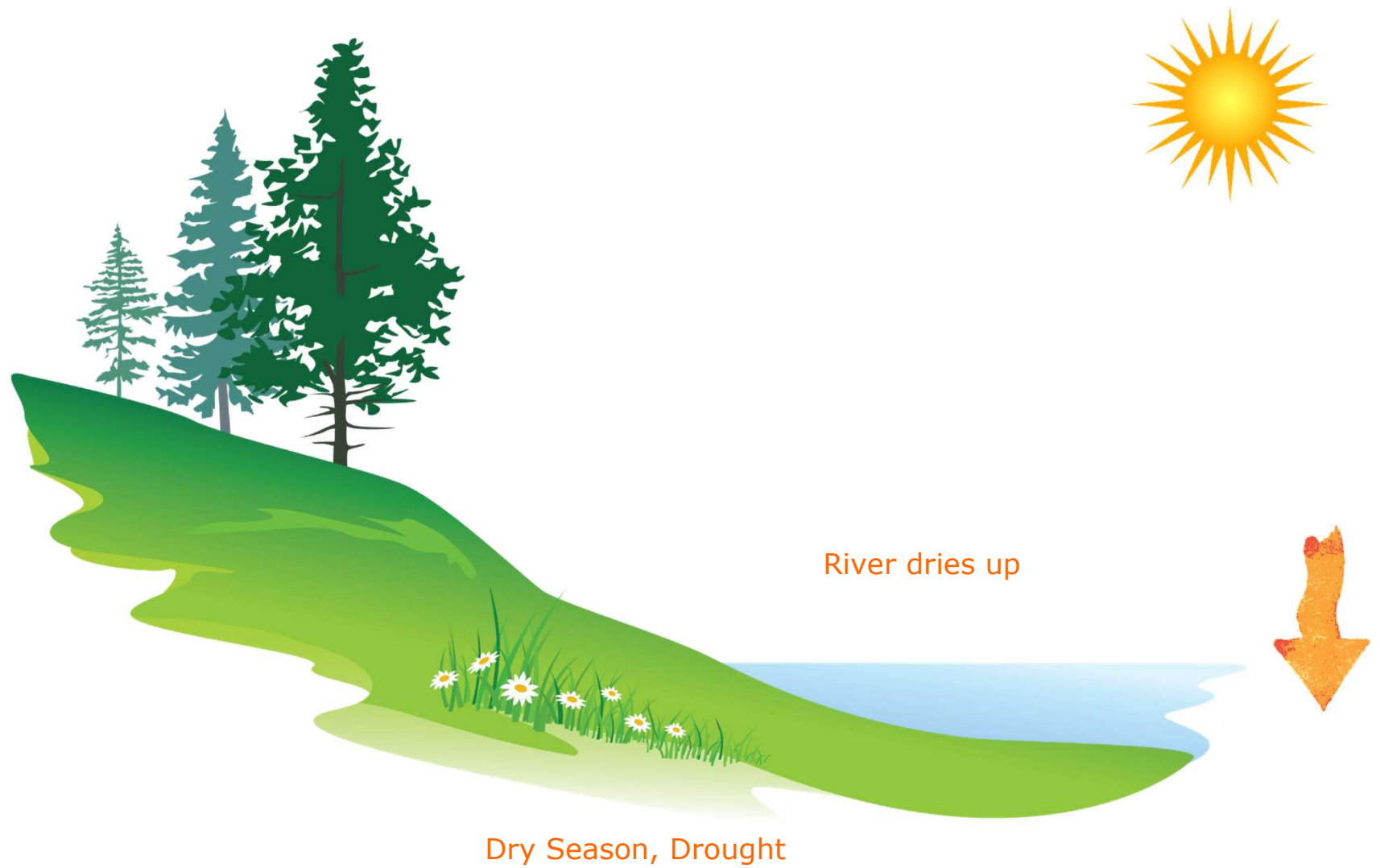


Filtering




Rainy Season/Accelerated Snow melt

Filtering

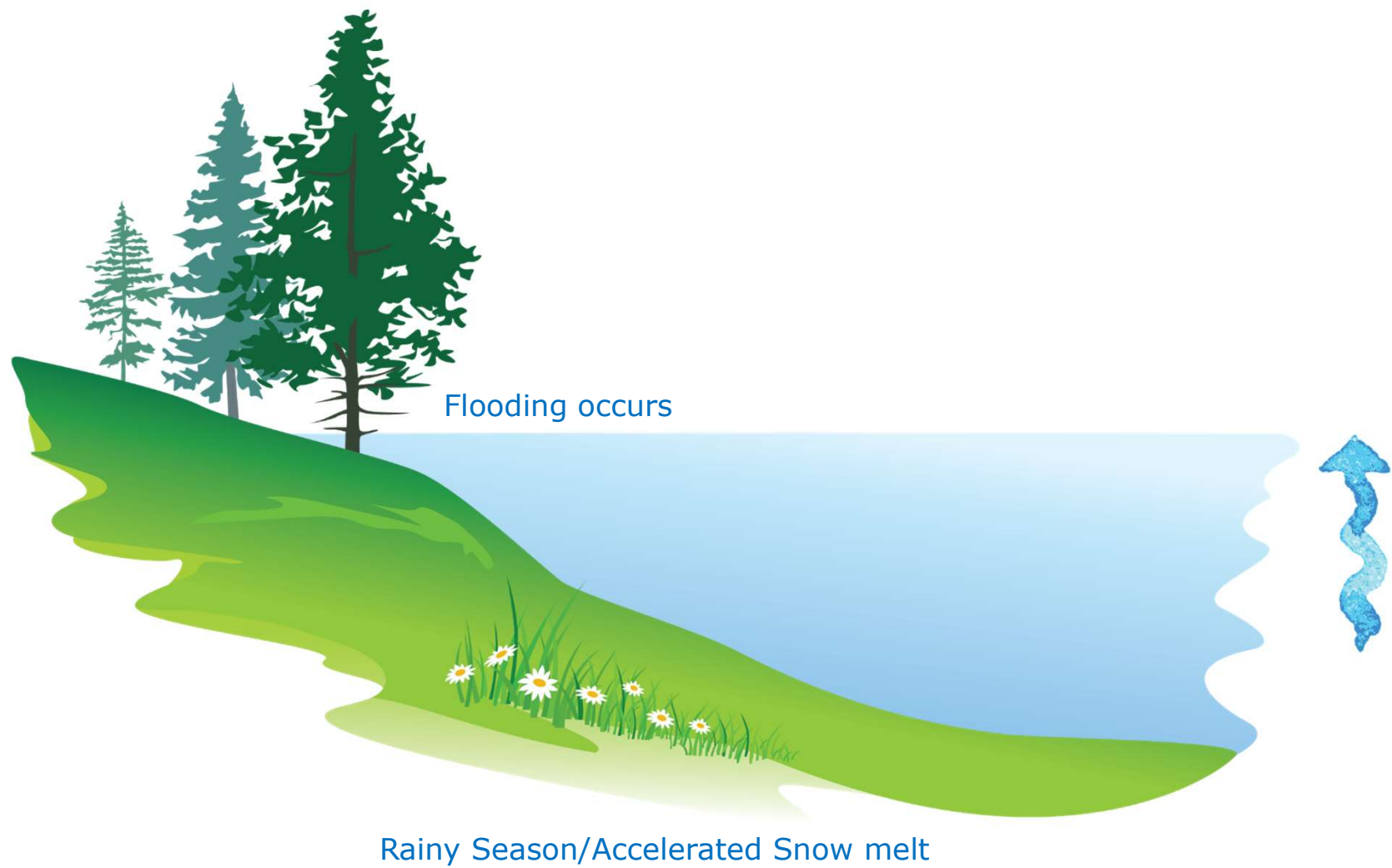


Filtering

WITH A DAM

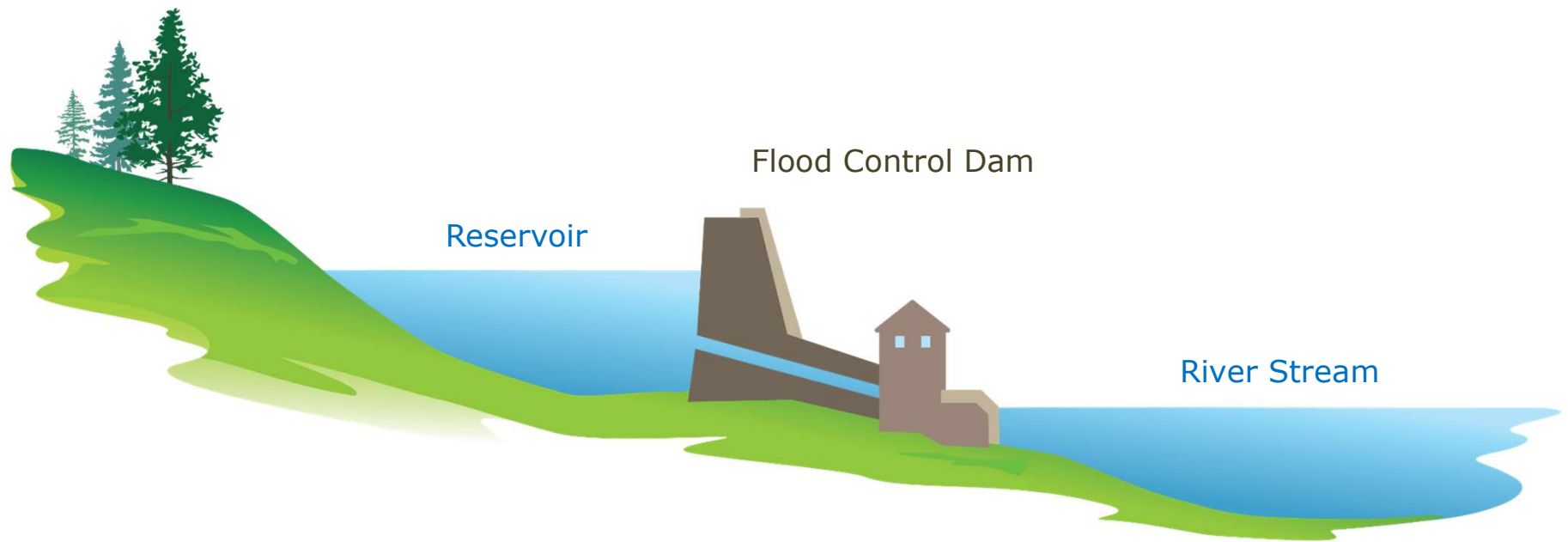

Filtering

WITH A DAM

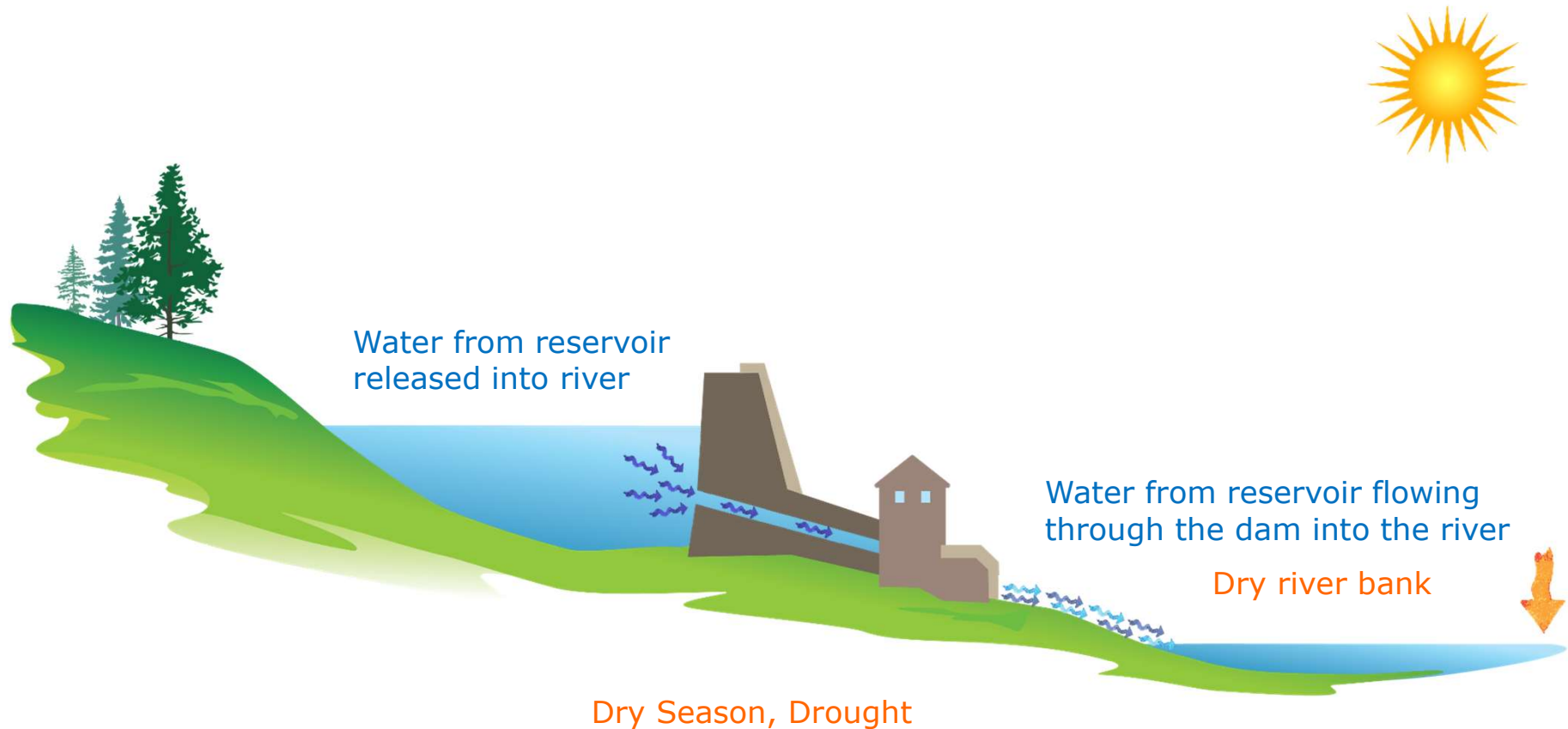


Filtering

WITH A DAM



Filtering

WITH A DAM

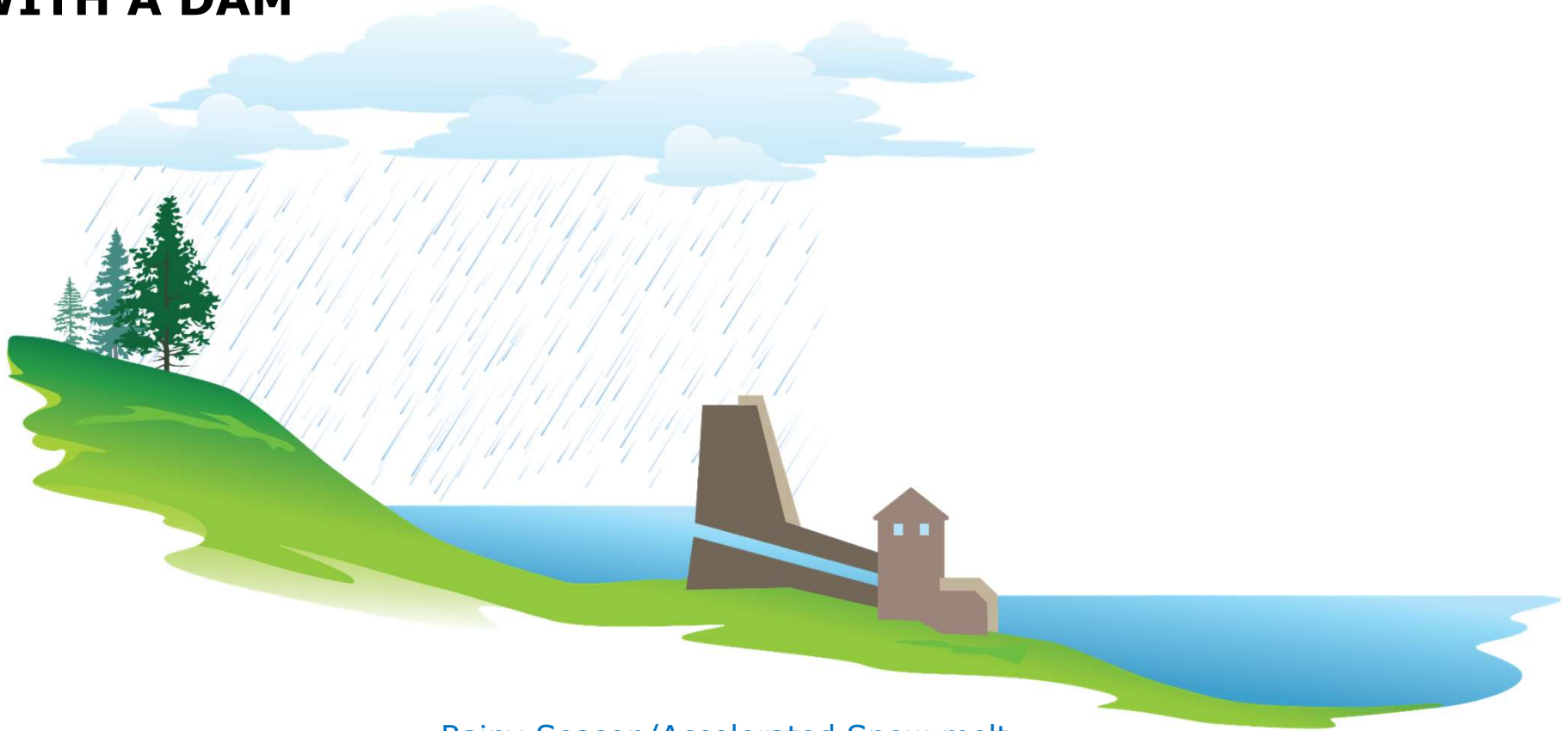

Rainy Season/Accelerated Snow melt

Filtering


WITH A DAM



RC Filters

- Low Pass Filters


Passive

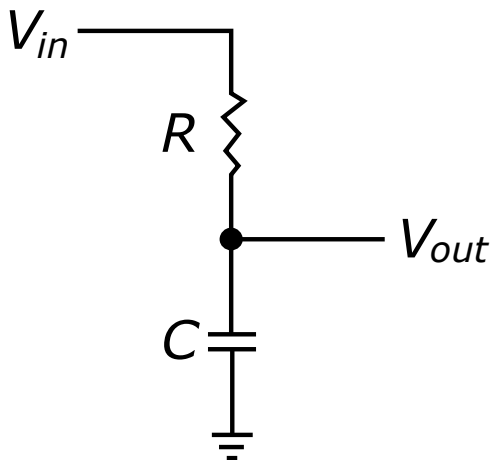

Passive low pass filter

$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi RC}$$

Active

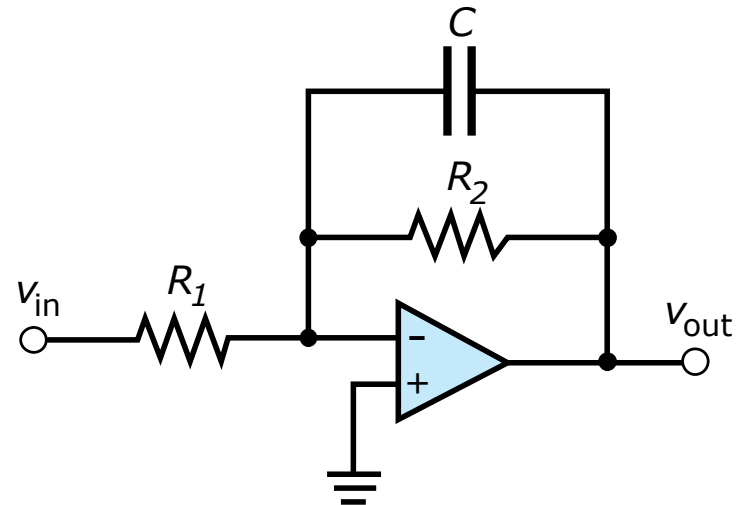


Active low pass filter

$$f_c = \frac{1}{2\pi R_2 C}$$

RC Filters

- High Pass Filters


Passive

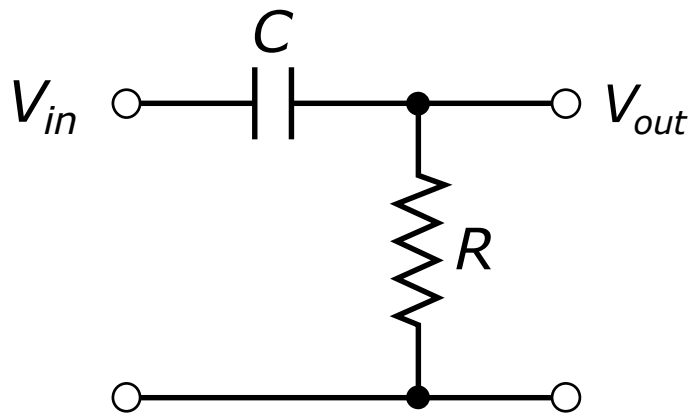

Passive high pass filter

$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi RC}$$

Active

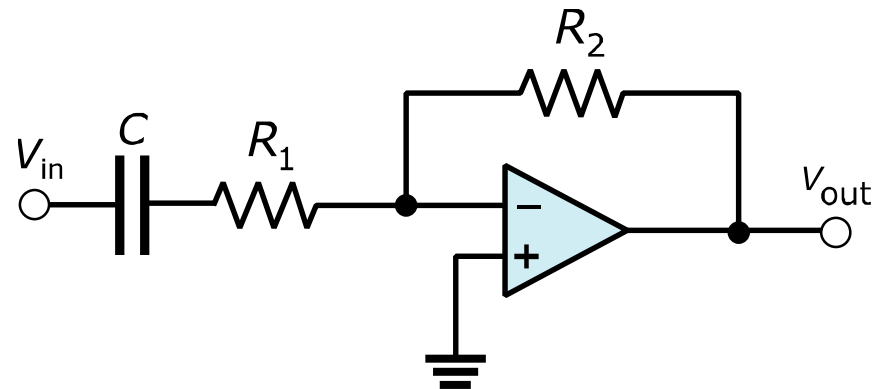


Active high pass filter

$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi R_1 C},$$

Filtering


- Band Pass & Band Stop Filters

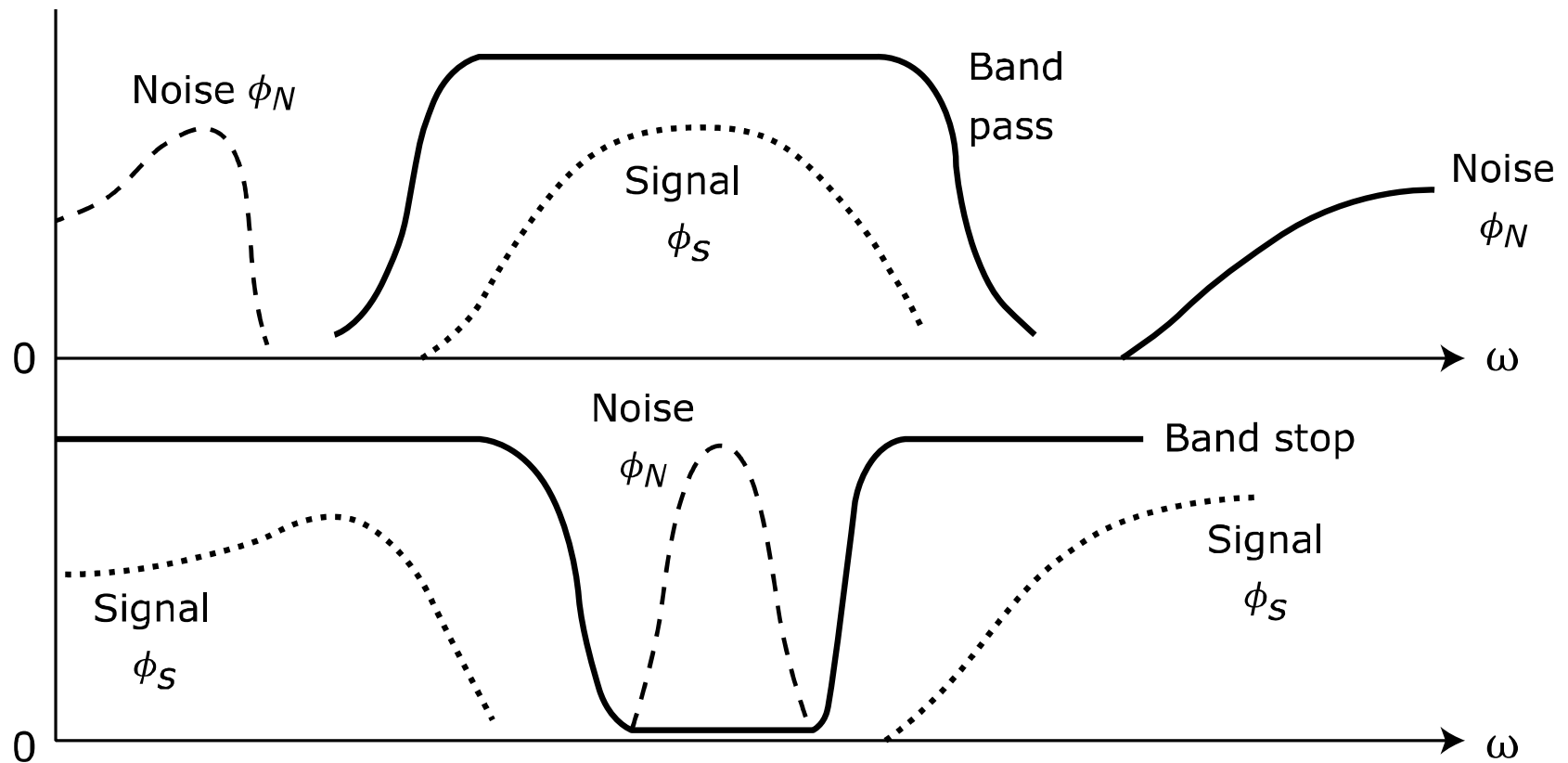

Band pass and band stop filters

Reducing Effects of Noise & Interference

- Averaging

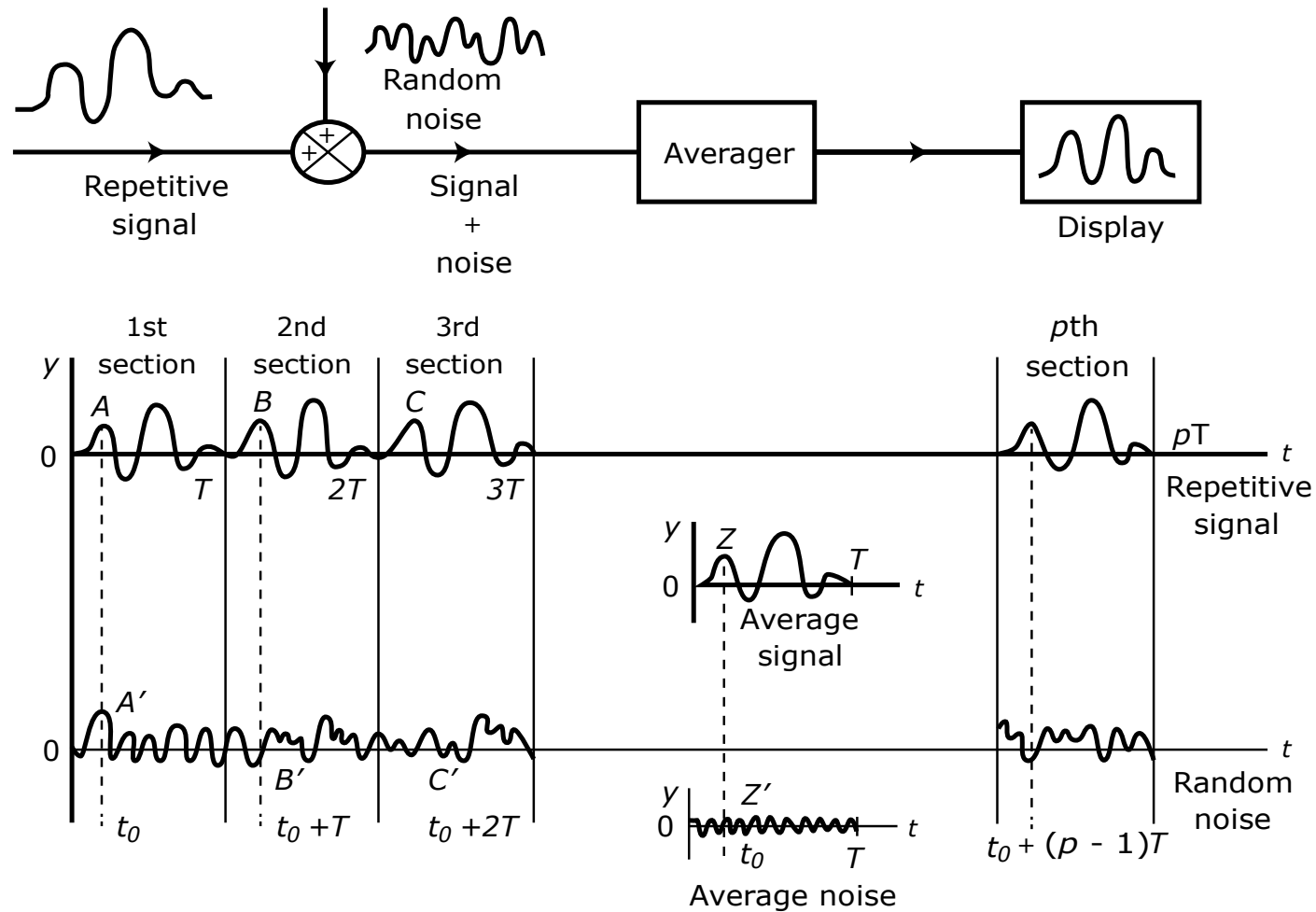

Reducing effects of noise and interference - averaging


Reducing Effects of Noise & Interference

- Averaging
 - For a repetitive measurement signal affected by random noise, suppose
 - It has a period T , a total of p cycles & N samples in each cycle, giving pN samples in total
 - For each sample, there are p number of corresponding samples from each cycle
 - The average value of the i^{th} sample is

$$y_i^{AV} = \frac{1}{p}(y_{i1} + y_{i2} + \dots + y_{ip}), \quad i = 1, \dots, N$$

Reducing Effects of Noise & Interference

- Averaging

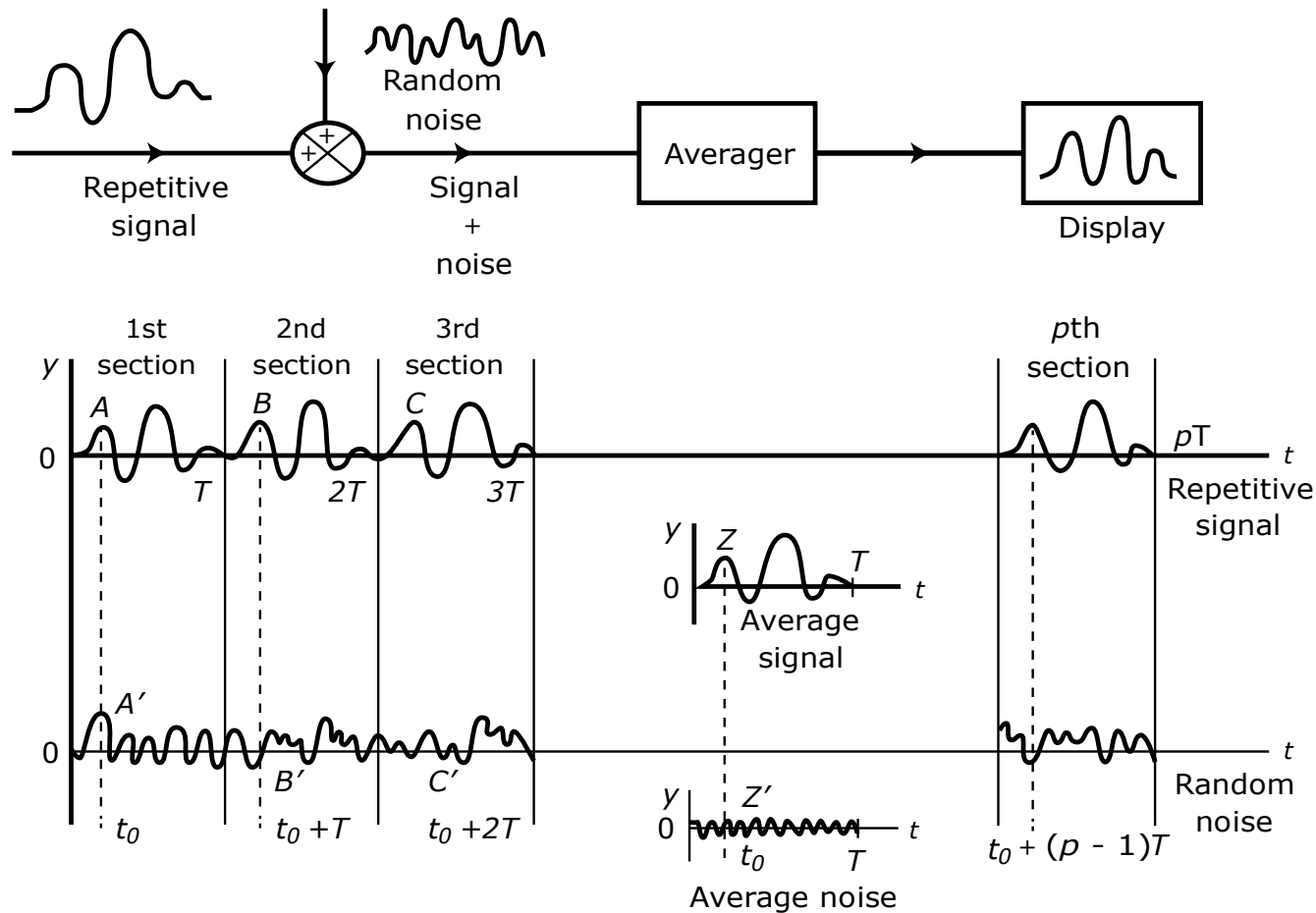


Reducing effects of noise and interference - averaging

$$y_i^{AV} = \frac{1}{p} (y_{i1} + y_{i2} + \dots + y_{ip}), \quad i = 1, \dots, N$$

Output Signal Conditioning Elements

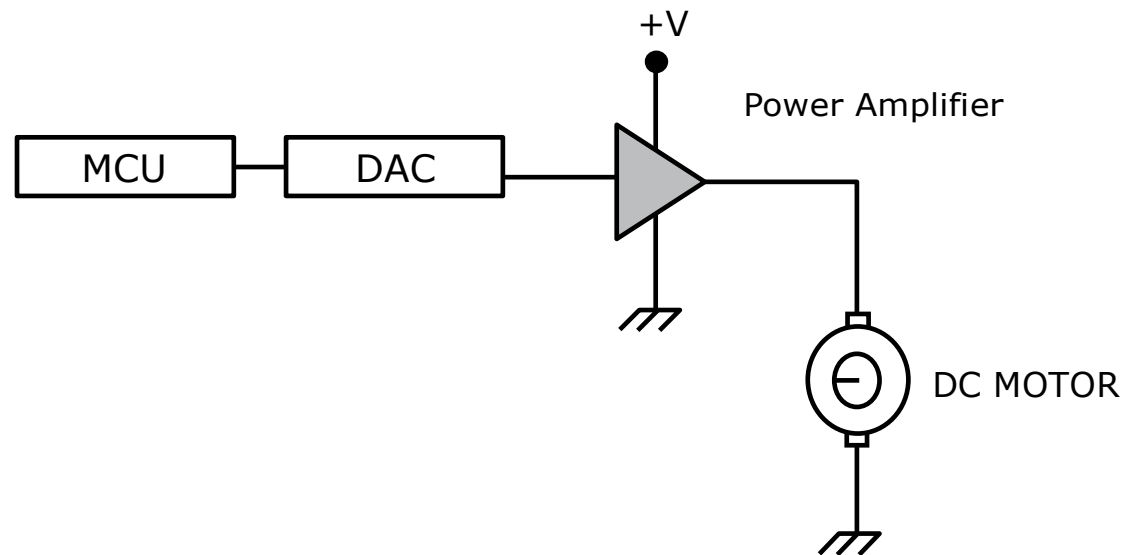
- Purpose
 - To convert the output of MCU into a form suitable for interfacing with the output devices
- Suitable forms
 - Analog signal: voltage or current
 - Higher voltage
 - Higher current
 - Alternating current



Output signal conditioning elements

Digital-to-Analog Converter

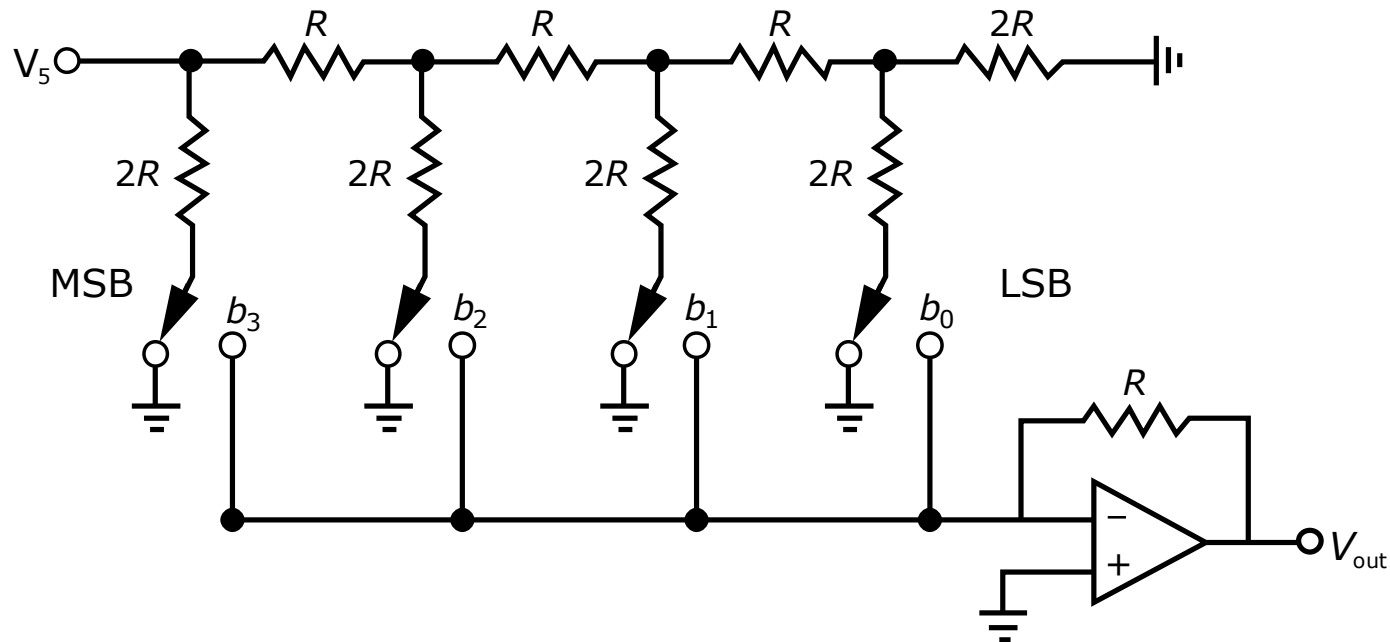
- Simplest type of DAC is a resistor ladder network connected to an inverting op amp circuit



Resistor ladder network connected to an inverting op amp circuit

Digital-to-Analog Converter

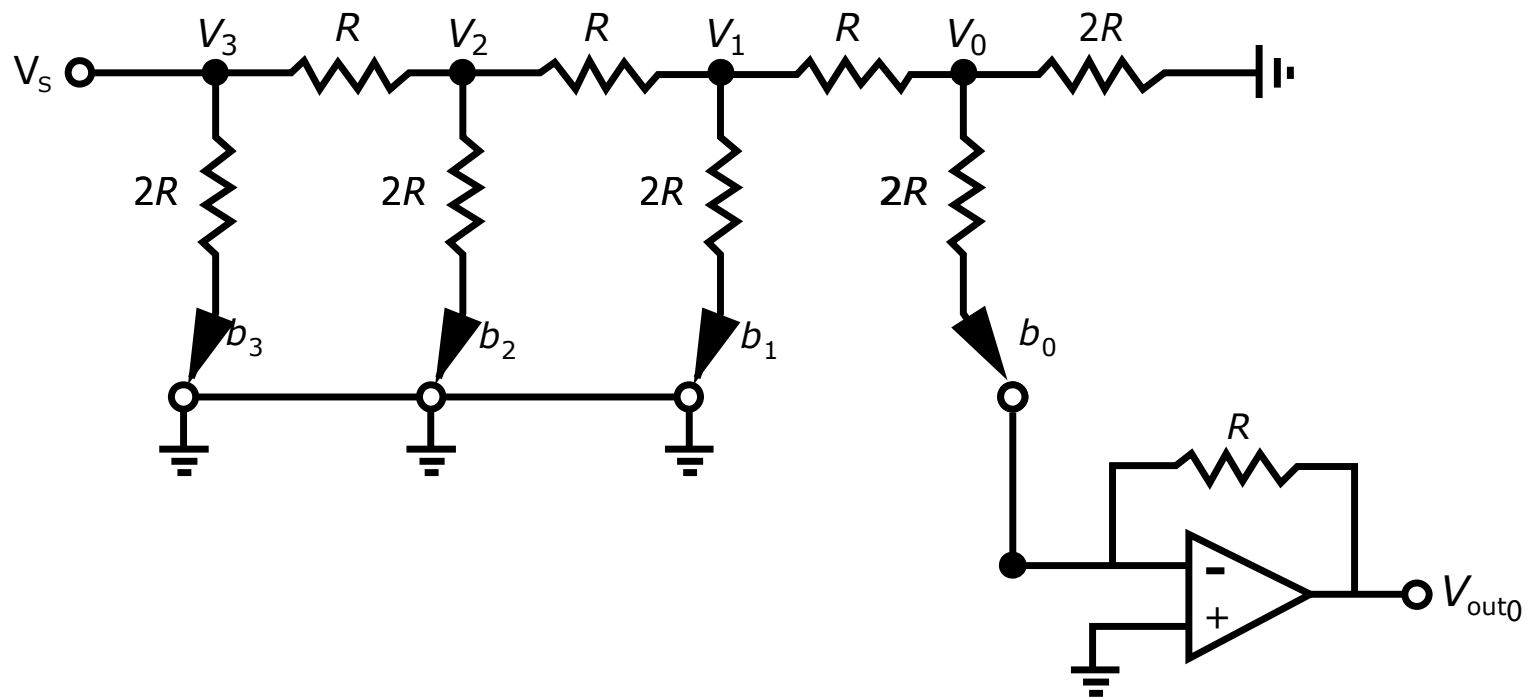- Consider a 4-bit output 0001
- Analog circuit equivalent:



4-bit output: analog circuit equivalent


Digital-to-Analog Converter

- Using voltage division,

$$V_0 = 0.5V_1; V_1 = 0.5V_2 \text{ and } V_2 = 0.5V_3$$

- Therefore, $V_0 = 0.125V_3 = 0.125V_s$
- V_0 is the input to the inverting op amp, which has a gain of $-R/2R = -0.5$
- Therefore, the analog output voltage of input 0001 is

$$V_{out0} = -0.0625V_s$$

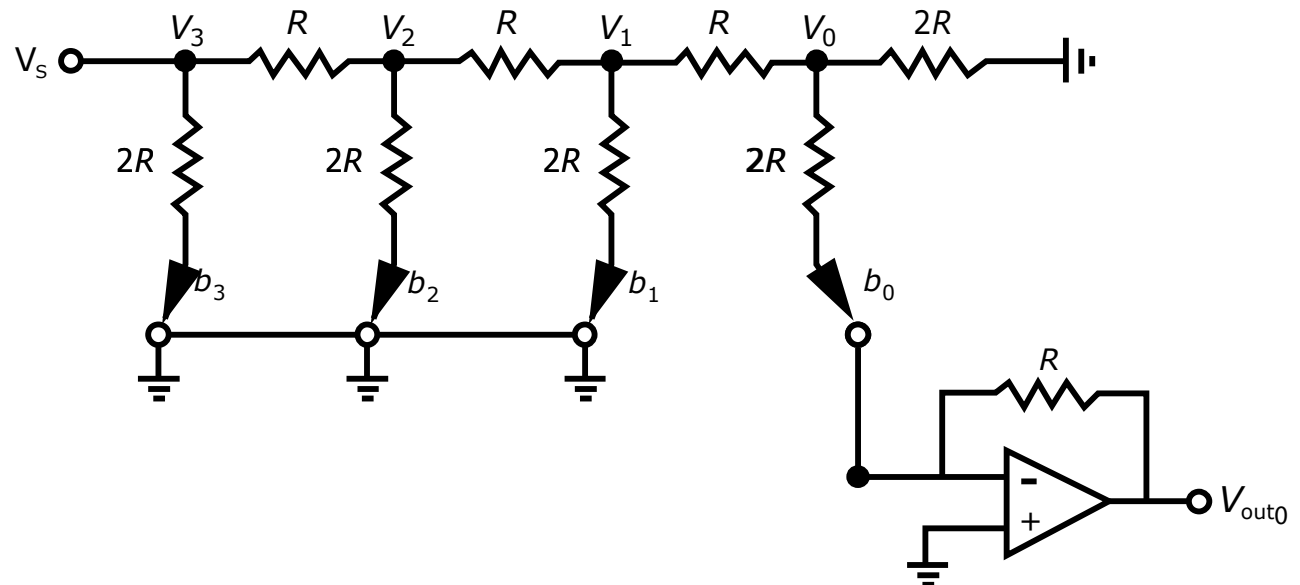


4-bit output: analog circuit equivalent

Digital-to-Analog Converter

- Analog output voltage of input
 - 0010 is $V_{out_1} = -0.125 V_s$
 - 0100 is $V_{out_2} = -0.25 V_s$
 - 1000 is $V_{out_3} = -0.5 V_s$
- The output for any combination of the four bits is
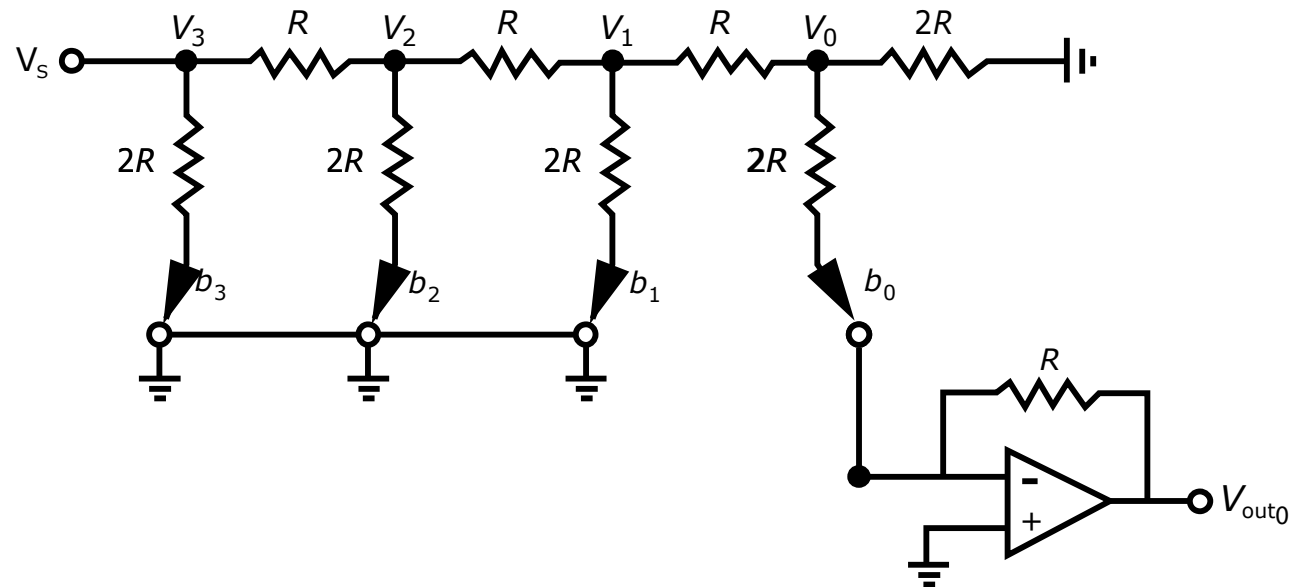
$$V_{out} = b_3 V_{out_3} + b_2 V_{out_2} + b_1 V_{out_1} + b_0 V_{out_0}$$



4-bit output: analog circuit equivalent

Summary

- Signals & Noise
 - Deterministic vs random signals
 - Noise characteristics & sources
 - Signal-to-Noise Ratio
- Input Signal Conditioning
 - Deflection Bridge: Quarter, Half, Full
 - Op-amps: Inverting, non-inverting, differential, voltage follower, voltage adder
 - Filters: Low Pass, High Pass, Band Pass, Band Stop
 - Averaging
- Output Signal Conditioning
 - Digital-to-Analog Converter