

Lecture 1

Mechanics Definition

-Stiffler: "Science that integrates mechanical devices with electronic controls"
-Bolton: "Integration of electronics, control engineering and mechanical engineering"
-Bradley, et al: "An integrating theme within the design process [combining] electronic engineering, computing and mechanical engineering"

-Shetty & Kolik: "Methodology used for the optimal design of electromechanical products"

-Auslander & Kempf: "The application of complex decision making to the operation of physical systems"

Measurement Systems

Transducer: a device to convert a physical quantity into a time varying voltage (called analog signal)

Signal Processor: a device to modify the analog signal

Recorder: a device to display or record the signal.

Linearity:

$$V_{out}(t) - V_{out}(0) = \alpha(V_{in}(t) - V_{in}(0))$$

Fundamental freq.:

$$\omega_0 = \frac{2\pi}{T} = 2\pi f_0$$

Fourier Series:

$$F(t) = C_0 + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t) + \sum_{n=1}^{\infty} B_n \sin(n\omega_0 t)$$

Where,

$$A_n = \frac{2}{T} \int_0^T f(t) \cos(n\omega_0 t) dt$$
$$B_n = \frac{2}{T} \int_0^T f(t) \sin(n\omega_0 t) dt$$
$$C_0 = \frac{1}{T} \int_0^T f(t) dt = \frac{A_0}{2}$$

Define:

$$C_n = \sqrt{A_n^2 + B_n^2}$$
$$\phi = -\arctan\left(\frac{B_n}{A_n}\right)$$

Then:


$$F(t) = C_0 + \sum_{n=1}^{\infty} C_n \cos(n\omega_0 t + \phi)$$

Bandwidth & Freq. Response:

$$dB = 20 \log_{10} \left(\frac{A_{out}}{A_{in}} \right)$$

-bandwidth \propto fidelity

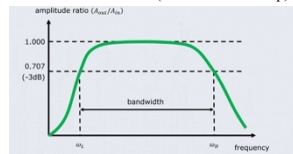-bandwidth = ω_L to ω_H (corner/cut-off freq.)



-3dB comes from

$$\frac{P_{out}}{P_{in}} = \left(\frac{A_{out}}{A_{in}} \right)^2 = \frac{1}{2}$$

Output amplitude:

$$A'_i = \left(\frac{A_{out}}{A_{in}} \right) A_i$$

Lecture 2

Periodic Function

$f(t+T) = f(t)$, T is period.

Even Function (Fully cosine waves)

$$f(-t) = f(t)$$

All $B_n = 0$

Odd Function (Fully sine waves)

$$f(-t) = -f(t)$$

All C_0 and $A_n = 0$

Complex Form

$$F(t) = \sum_{n=-\infty}^{\infty} D_n e^{jn\omega_0 t}$$

Where,

$$D_n = \frac{1}{T} \int_{-T/2}^{T/2} f(t) e^{-jn\omega_0 t} dt$$

Spectrum & Measurement

-important to estimate spectrum when choosing measurement


-ideal system replicates freq. of an input signal

-practical system limited

Error of Approximation

$$f(t) \approx \sum_{n=-N}^N D_n e^{jn\omega_0 t} = S_N(t)$$
$$\epsilon(t) = f(t) - S_N(t)$$
$$MSE = \frac{1}{T} \int_0^T \epsilon^2(t) dt$$

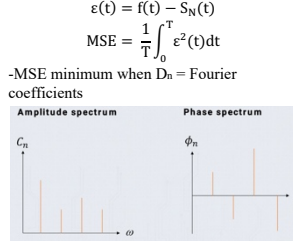-MSE minimum when D_n = Fourier coefficients



Fourier Series Conditions:

-f(t) is a single-value function

-for any t_0 , $\int_{t_0}^{t_0+T} |f(t)| dt < \infty$

-f(t) has a finite number of discontinuities

-f(t) has a finite number of maxima and minima

-f(t) amplitude function, fulfil 4 conditions

Insights

-how signals of diff. freq. represented in a signal

-easier & cost-eff. To characterise freq. content instead of time description of noise

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals


-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals

-diff. treatment of diff. parts of EM spectrum help you separate radio, tv and cell phone signals


First Order System

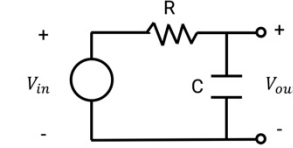

$$RC \frac{dV_{out}}{dt} + V_{out} = V_{in}$$
$$\tau \frac{dX_{out}}{dt} + X_{out} = KX_{in}$$
$$X_{out} = X_{out}(0)e^{-t/\tau} + KA_{in}(1 - e^{-t/\tau})$$
$$X_{out} = KA_{in}(1 - e^{-t/\tau})$$

-1 time constant \rightarrow 63.2%
-4 time constants \rightarrow 98%, assume steady state

Second Order System

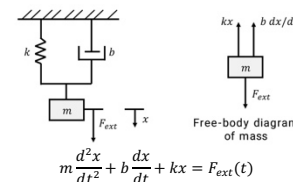

When $F_{ext} = 0$:
When $\zeta = 0$,
 $x_h(t) = A \cos(\omega_n t) + B \sin(\omega_n t)$

When $\zeta < 1$,
 $x_h(t) = e^{-\zeta \omega_n t} [A \cos(\omega_d t) + B \sin(\omega_d t)]$

When $\zeta > 1$,
 $x_h(t) = e^{-\zeta \omega_n t} [A \cosh(\omega_d t) + B \sinh(\omega_d t)]$

When $\zeta = 1$,
 $x_h(t) = (A + Bt)e^{-\omega_n t}$

Why Op-Amps?

-transducer signals too small

-transducer signals too noisy

-transducer signals contain wrong information and have DC offset due to design and installation of transducers

-low cost, versatile IC, consists of internal transistors, resistors & capacitors

-combine w/ ext. discrete components \rightarrow wide variety of signal processing circuits

-wide variety of signal processing circuits

-wide variety of signal processing circuits

-wide variety of signal processing circuits

-wide variety of signal processing circuits

Quantization Size/Zone Width:

$$Q = (V_{max} - V_{min})/N$$

$$N = 2^n$$

where, n is number of bits, N is number of states.

Quantizing & Encoding Process

1. Determine no. of zones & zone width

2. Assign midpoints of zones a value from 0 to N-1

3. Assign binary code to each zone (find no. of bits needed)

Quantising error:

-diff. btwn. actual and midpt.

-zones \uparrow , Q \downarrow , error \downarrow , bits required \uparrow , bitrate \uparrow

Ideal waveform = Quantized waveform + errors

Ideal waveform = Quantized waveform + errors

Ideal waveform = Quantized waveform + errors


Ideal waveform = Quantized waveform + errors

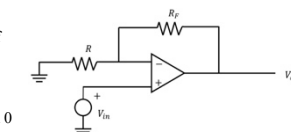Non-Inverting Amplifier (amplifies input signal without inverting)




$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R}$$

Summer Amplifier (add analog signals)

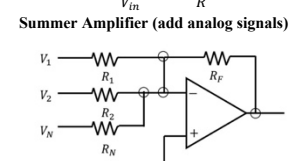


$$V_{out} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \dots + \frac{R_f}{R_N} V_N \right)$$

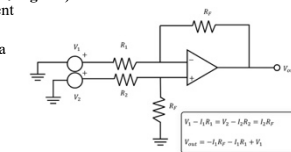Difference Amplifier (subtract analog signals)




$$V_{out} = V_1 - \left(\frac{R_2}{R_1} + \frac{R_4}{R_3} \right) V_2$$

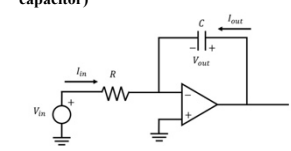Integrator (replace feedback resistor w/ capacitor)



$$V_{out}(t) = -\frac{1}{RC} \int_0^t V_{in}(\tau) d\tau$$

Practical Integrator

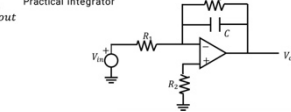


$$C \frac{dV_{out}}{dt} + \frac{V_{out}}{R_s} = I_{out} = -I_{in} = -\frac{V_{in}}{R_1}$$

$$\frac{dV_{out}}{dt} + \frac{V_{out}}{CR_s} = -\frac{V_{in}}{CR_1}$$

Should choose:


$$R_s > 10R_1, \quad R_2 = -\frac{R_1 R_s}{R_1 + R_s}$$

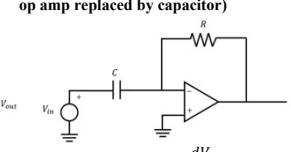Differentiator (input resistor of inverting op amp replaced by capacitor)



$$V_{out} = -RC \frac{dV_{in}}{dt}$$

Sample & Hold

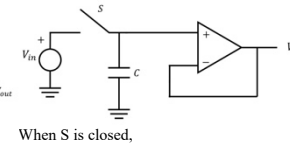

$$V_{out}(t) = V_{in}(t)$$

When S is open,

$$V_{out}(t - t_{sampled}) = V_{in}(t_{sampled})$$

-choose C w/ low leakage

-used for ADC

-signal value must be stabilised

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

-voltage-holding capacitor and voltage

Sensors

-transducer: convert one form of energy to another
-sensors: produce (electrical) output signal for sensing a physical phenomenon


Classification

-analog vs digital
-passive (no ext. power, draw from input signal) vs active
-null (deflection due to measured quantity is balanced) vs deflection
-subject of measurement: mechanical, optical, thermal etc.

Instrumentation Systems


-sensing module: electro + mechanical/thermal/optical/pyro/piezo
-conversion module: analog → digital
-pre-processing: variable manipulation module
-data transmission: wired/wireless, over the web
-presentation/storage: to final user

Basic Concepts

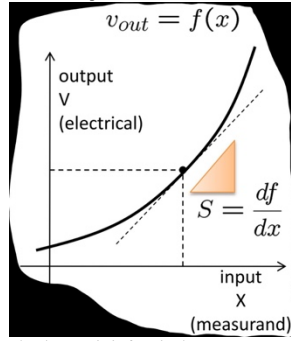

I/O characteristic function/response:
input → stimulus or measurand (temp, pressure, strain)
Output → electrical signal (voltage, current, freq, phase)

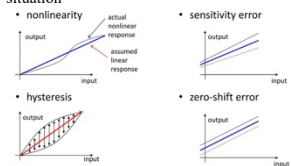-sensitivity S : output variation/input variation, $S = df/dx$
-resolution: minimum change of the measurand that can be reliably detected, limited by noise, bit-conversion
-accuracy: difference of measurement from true value, %FS, full scale
-repeatability: how well a system/device can reproduce an outcome in unchanged situation




Resistance Temperature Detector (RTD)

-based on changes of resistance w/ temp.
-metal wire on insulating support → eliminate mechanical strain
-encasing → minimize environment influence
-linear for limited range:

$$\frac{R}{R_0} = 1 + \alpha(T - T_0)$$

Wheatstone Bridge

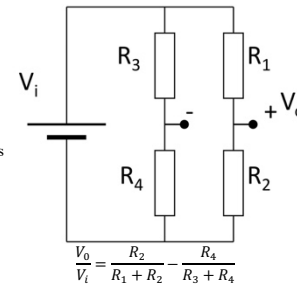


$$V_0 = 0 \Leftrightarrow R_1 R_4 = R_2 R_3$$


Thermistors

-ceramic like semicons.
-resistance decreases w/ temp.
-high sensitivity, ruggedness, fast time-response

$R = R_0 e^{\beta(\frac{1}{T} - \frac{1}{T_0})}$
Resistive Sensors (Potentiometer, pot)
-3 terminal electro-mech. device based on a conductive wiper against fixed resistive element
-many varieties: rheostats, trimmers, volume control
-precision potentiometers: manually/digitally tuneable
Linear Variable Differential Transformer (LVDT)
-type of transformer
-measures linear displacement
-variable coupling via sliding ferromagnetic core
-differential voltage:
 $V_{out} = \Delta V = V_2 - V_1 \approx x(t)V_0$

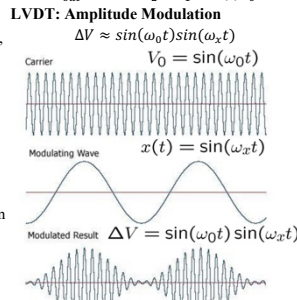

LVDT: Amplitude Demodulation

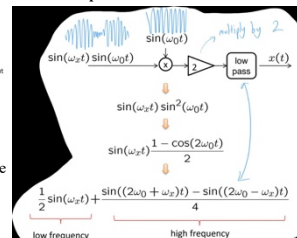


Capacitive Sensor (proximity sensor)

- $C = Q/V$
-ideal case: infinite parallel plates
Gauss' Law: $Q = \iint \epsilon_0 \epsilon_r E dS$
 $C = \frac{Q}{V} = \frac{\epsilon_0 \epsilon_r S}{d}$

Guard Electrode

-limit field-fringing effects

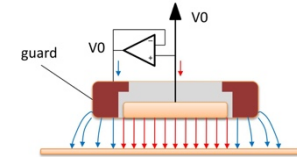

AC Interfacing

-AC bridge, AC driving, modulation

Hall Effect

-Lorentz Force:

$$\vec{F} = q \vec{v} \times \vec{B}$$


-Lorentz's Law:

$$\vec{F} = (i \times \vec{B}) L$$


-used for contactless proximity sensor, current sensor

Light Detectors

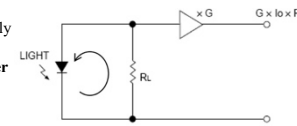
-photo-resistors
-photo-diodes: load resistance



-photo-diodes: op-amp

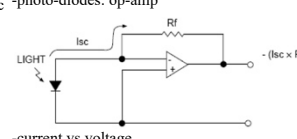


-current vs voltage

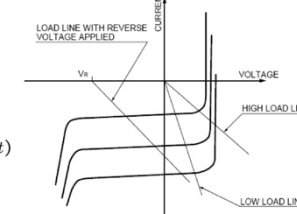

Encoders

-digital encoders: convert motion (linear/rotary) → digital pulses (optical transmitter/receiver pairs – glass/plastic material photographically patterned)
-Hall effect sensors + magnetic rings/bars
-incremental encoders w/ 2 Tx/Rx pairs – encoding steps + direction; simple design, needs a 'reset' position
-absolute encoders n Tx/Rx pairs for coding 2^n sectors; more expensive; spurious states may arise from contemporary transitions, solved using gray code as only bit changes every time

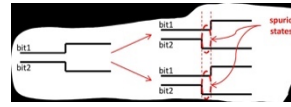

Inductive Kickback

Motors

-EM induction using LHR:

$$emf = E = -\frac{d\Phi}{dt}, \Phi = \int \vec{B} d\vec{S}$$

-Faraday's Law:

emf = electro-motive-force

Φ = magnetic flux

Σ = surface whose boundary coincides w/ the coil

DCM Structure

-stator: external, fixed
-rotor: internal, rotates
-stator and rotor fields always orthogonal → maximum torque

-w/ commutation: maintains unstable equilibria → constant motion

-w/o commutation: there is a stable equilibria → motion ceases

-more poles, more constant torque i.e., independent of rotor positions

Equations

Armature Eqn:

$$V = Ri + L \frac{di}{dt} + e$$


Mechanical eqn:

$$J\dot{\omega} + b\omega = T_e - T_L$$

Coupling:

$$\begin{cases} T_e = K_t i \\ e = K_e \omega \end{cases}; \quad T_e \omega = ei; \quad K_e = K_t \triangleq K_a$$

DCM Speed-Torque Curve

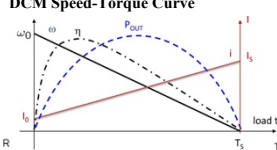

Power:

$$P_{out} = \omega T_L$$

$$P_{out}^{max} = \frac{1}{4} \omega_0 T_s$$

Friction load:

$$T_L = b_L \omega_L$$

Constant torque:

$$T_L = \text{const.}$$

Inertial:

$$T_L = I \frac{d\omega}{dt} = 0$$


Loads can be a combination of above 3 ↑

Efficiency:

$$\eta = \frac{\text{power out}}{\text{power in}} = \frac{\omega T_L}{VI}$$

Driving DCM

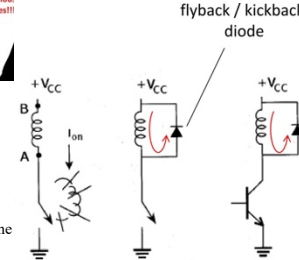-avoid power amp. beuz large power dissipation + over-heating of amp.
-continuously switch the motor on and off, Pulse Width Modulation (PWM)
-DCM is a 2nd order low pass filter



Steady-state I_{on} cannot immediately go to 0 when the switch is opened. Changing current induces a voltage across the inductor, making potential at A > B, causing the switch to blow up. Kickback/flyback diode protects the switch (physical/transistor) from blowing up.

DC Brushless Motors

-stator field rotating
-rotor field given by permanent magnet
-keep rotor and stator field orthogonal to maximize output torque
-detect rotor position via encoders (Hall effect sensors)
-select appropriate switches to determine desired torque

Strain Gauges

-determine safe loading conditions of mechanical structures

Electrical Resistance Strain Gauges

-thin metal (constantan) foil, patterned onto plastic backing material, bonded onto mech. structures, stress derived using solid mech.
-strain, $S = dL/L$, +ve if tensile, -ve if compressive

-Poisson's ratio: $\nu = \frac{\text{lateral strain}}{\text{axial strain}}$

-resistance, $R = \rho \frac{L}{A}$

-rectangular conductor:

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - \left(\frac{dw}{w} + \frac{dh}{h} \right)$$

-axial strain, $S = dL/L$

-lateral strain:

$$\frac{dw}{w} = \frac{dh}{h} = -\nu \frac{dL}{L} = -\nu S$$

Combining above eqns.,

$$\frac{dR}{R} = \frac{d\rho}{\rho} + S + 2\nu = \left(\frac{d\rho}{\rho} + 1 + 2\nu \right) S$$

$$\frac{dR}{R} = GS$$

FYI:

$$\text{piezoresistivity} = \frac{d\rho}{\rho} \frac{1}{S}$$


Transverse Sensitivity

$dR = R_0 GS$
-the larger R_0 , the larger dR
-long and thin wires allow R_0 , wires must be aligned w/ axial strain S^a
-serpentine wires
-end loops: aligned w/ transverse axis, made thicker to reduce sensitivity to S^t


Materials

-best materials: constantan, ferrous alloys
-typical strain ranges S : $1-10^4 \mu S$, G : 2
-challenge: detecting small resistance changes

Wheatstone bridge: 1st order approx.:

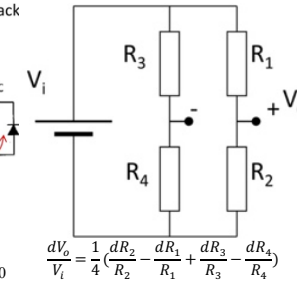

Quarter-bridge

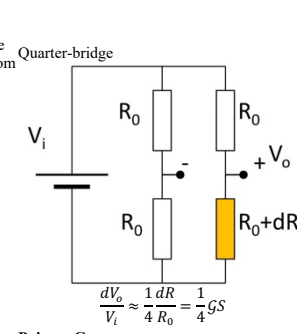


Poisson Gauge

$$\frac{dV_0}{V_i} = \frac{1}{4} G(1 + \nu)S$$


Half Bridge

-two active strain gauge

-bending:

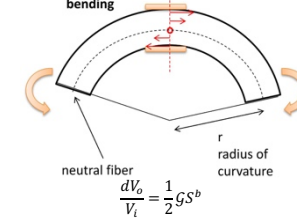

-axial loading:
axial loading

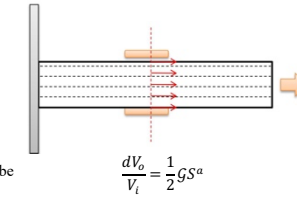

Apparent Strain:

-combinations of different mechanical loading
-e.g. beam under bending and axial loading:

$$S_1 = S^a + S^b$$

$$\text{Bottom of beam: } S_1 = S^a - S^b$$

Different electrical configuration:

