

# **CG1111A: Engineering Principles & Practice I**

Basics of Operational Amplifiers




# Learning Outcomes

Understand:

- How op-amps **operate**
- The difference between **inverting** and **non-inverting** amplifiers
- How to adjust the **amplification gains** of inverting & non-inverting amplifiers
- How to **analyze** circuits containing op-amps
- The **practical considerations** of op-amp circuits
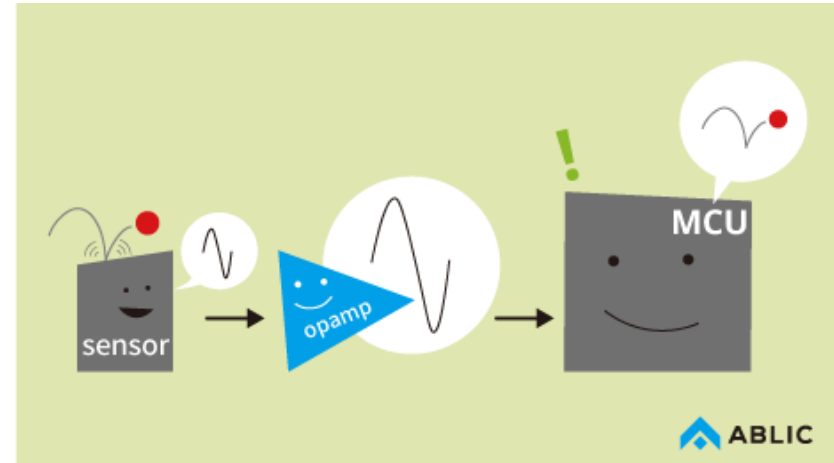
# What is an “Operational Amplifier”?


- An “operational amplifier (**op-amp**)” is an integrated circuit that can amplify weak electric signals




Credit: Image from ablic.com

- It has **two input** signal terminals and **one output** signal terminal
- It amplifies and outputs the **voltage difference** between the two input terminals

# Op-Amp Terminals


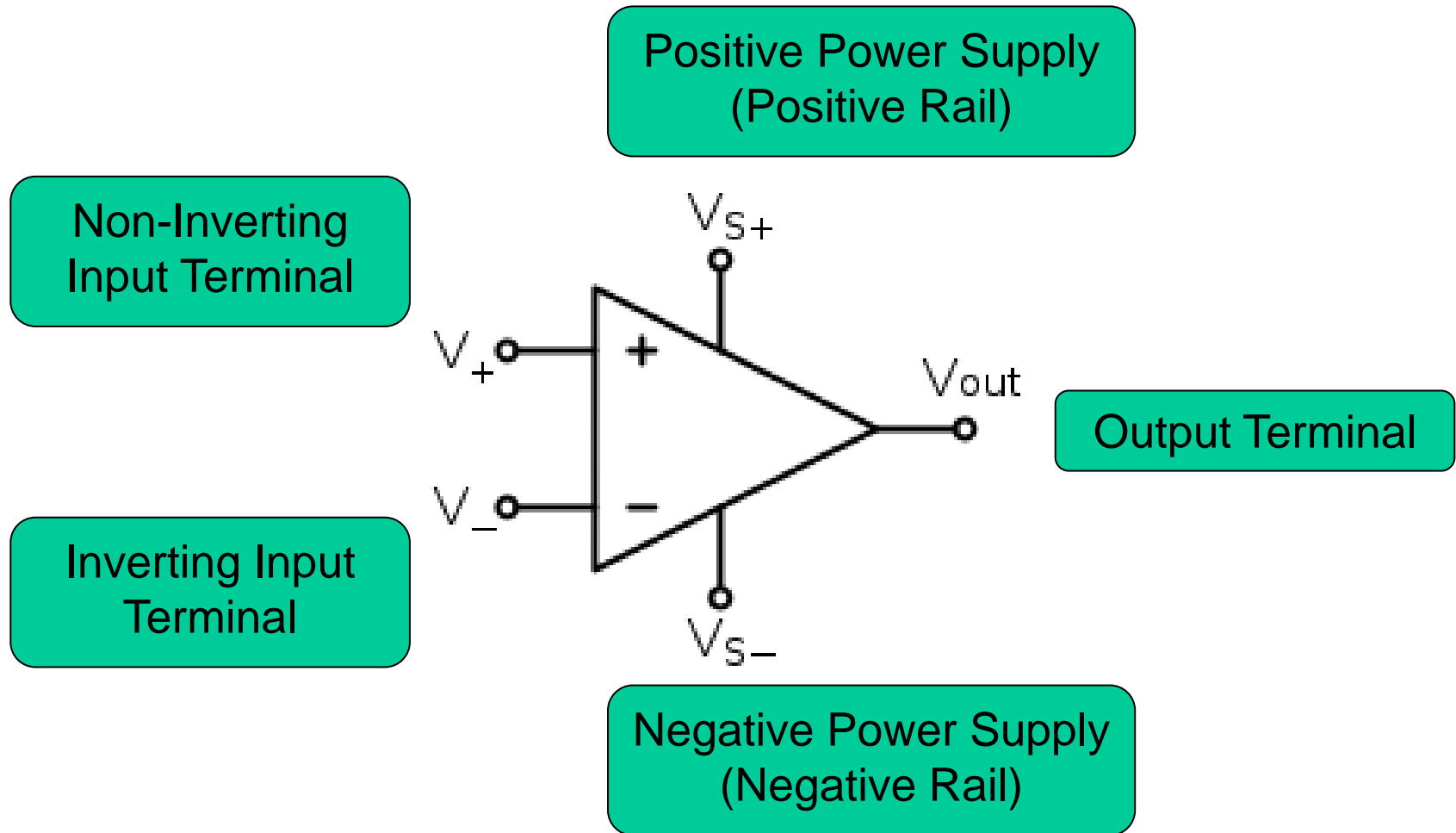


# Op-Amp Equivalent Circuit

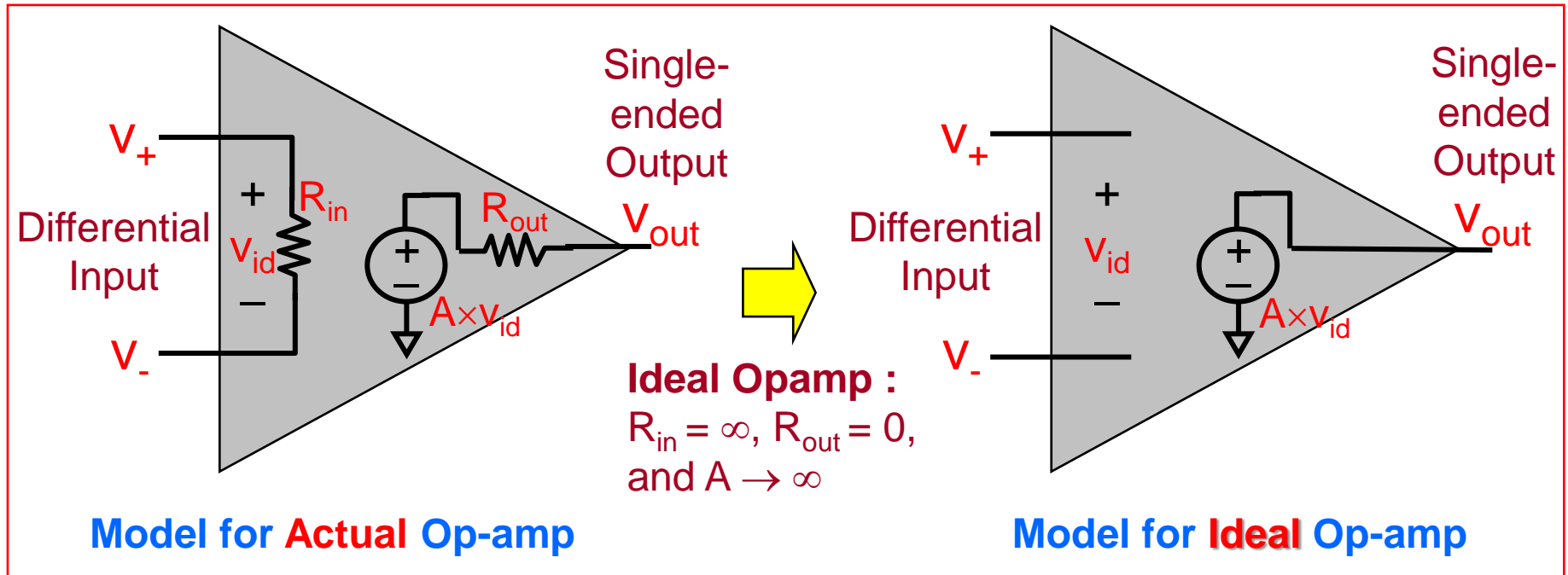

- **$A$**  is the open-loop voltage gain  
–It is very large, approaching infinity
- **$R_{in}$**  is the input impedance (very large) &  **$R_{out}$**  is the output impedance (very small)
- To **simplify** analysis, we always assume **infinite  $R_{in}$**  and  **$A$** , and **zero  $R_{out}$**

# What is an Op-amp IC Chip?

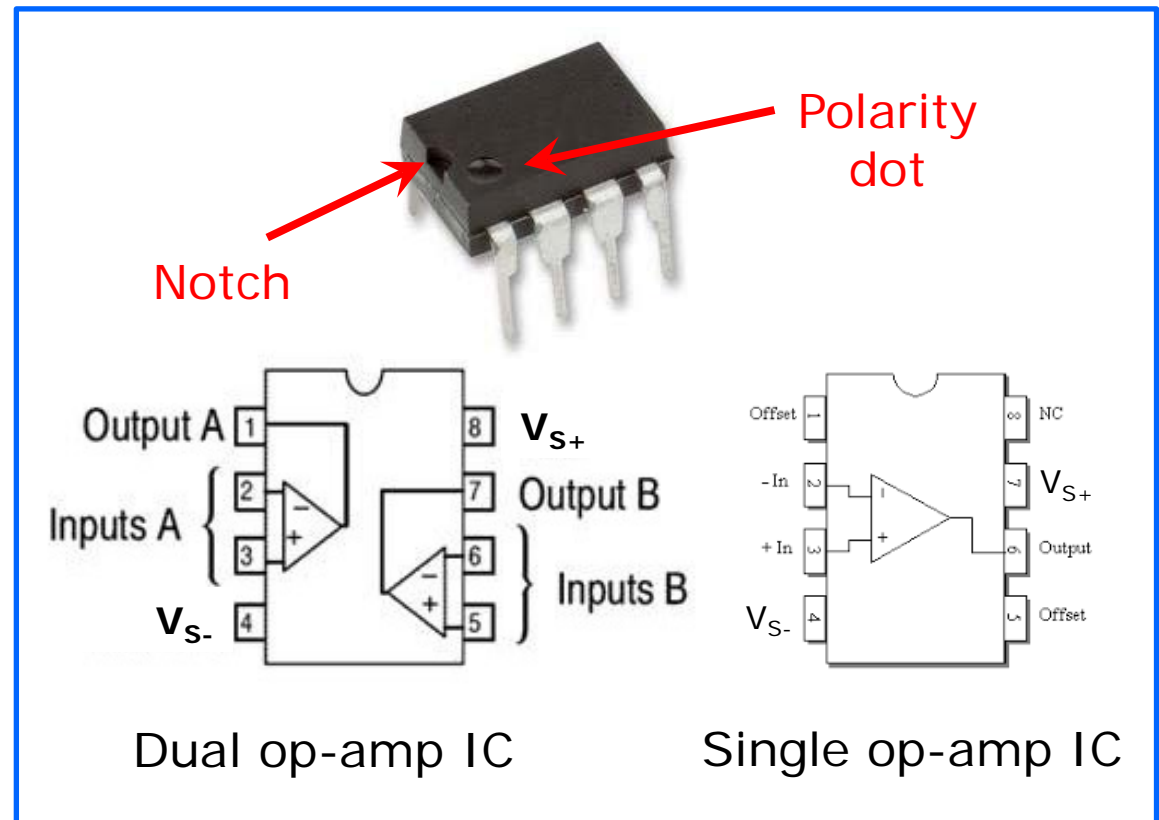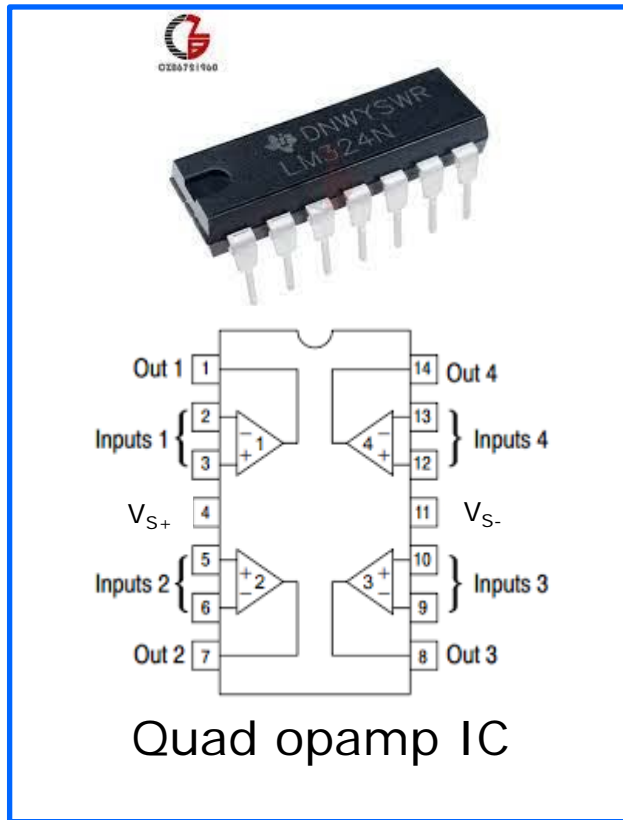

- Notch or polarity dot indicate the location of pin 1
- Quad and dual op-amp IC have 4 and 2 independent op-amps on the same chip sharing the same supplies ( $V_{S+}$  and  $V_{S-}$ )

# How to Read Its Datasheet?

**Single supply:** MIN: 3 V  
MAX: 30 V  
**Dual supply:** MIN:  $\pm 1.5$  V  
MAX:  $\pm 15$  V

			MIN	MAX	UNIT	
V <sub>S</sub>	Supply voltage, V <sub>S</sub> = ([V+] – [V–])	LM358B, LM358BA, LM2904B, LM2904BA	3	36		
		LM158, LM258, LM358, LM158A, LM258A, LM358A, LM2904V	3	30	V	
		LM2904	3	26		
PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
INPUT IMPEDANCE						
Z <sub>ID</sub>	Differential		10    0.1			MΩ   pF
OPEN-LOOP GAIN						
A <sub>OL</sub>	Open-loop voltage gain	V <sub>S</sub> = 15 V; V <sub>O</sub> = 1 V to 11 V; R <sub>L</sub> ≥ 10 kΩ, connected to (V–)	70	140		V/mV
			T <sub>A</sub> = –40°C to +85°C	35		V/mV
R <sub>O</sub>	Open-loop output resistance	f = 1 MHz, I <sub>O</sub> = 0 A		300		Ω

▪ <https://www.ti.com/lit/gpn/lm358>

140 V/mV = 140000


- Identify the key parameters, such as  $V_S$  (Supplies),  $A_{OL}$  (Gain),  $Z_{ID}$  (Input Impedance) and  $R_O$  (Output Impedance)
- Parameters are obtained with certain test conditions
- MIN, TYP, MAX specify either allowable range (e.g.,  $V_S$ ), or potential parameter fluctuations (e.g.,  $A_{OL}$ )
- **Unit is important** for all engineering parameters

# Typical Op-amp Parameters

Parameter	Variable	Typical Ranges	Ideal Values
Voltage Gain	$A$	$10^5$ to $10^8$	$\infty$
Input Impedance	$R_{in}$	$10^5$ to $10^8 \Omega$	$\infty \Omega$
Output Impedance	$R_{out}$	A few tens to a few hundreds $\Omega$	$0 \Omega$
Supply Voltage	$V_{S+}$ or $V_{CC}$ $V_{S-}$ or $V_{EE}$ or $-V_{CC}$	3 to 30 V -30 to 0 V	N/A N/A



# How to Analyze Op-amp Circuit?

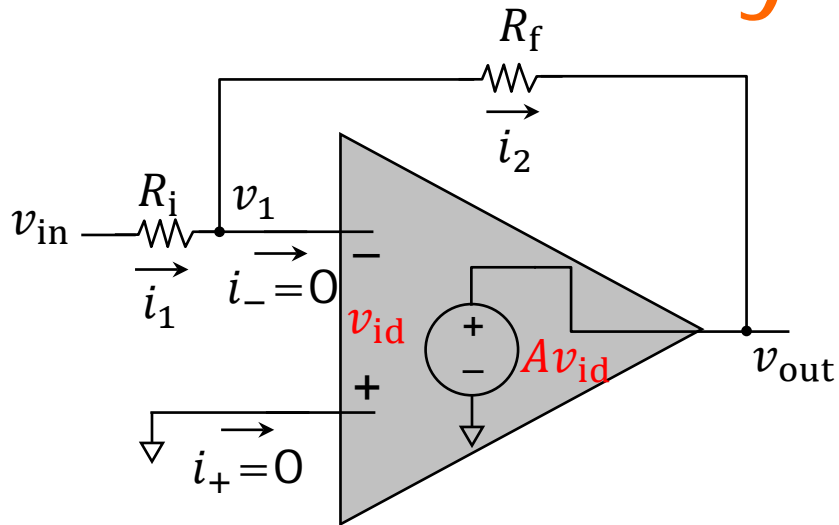

## “Transfer Function” for Op-amp Circuit

$$v_{id} = 0 - v_1 \quad \text{and} \quad v_{out} = A v_{id} = A(-v_1)$$

$$\Rightarrow v_1 = -\frac{v_{out}}{A}$$

$$\frac{v_{in} - v_1}{R_i} = \frac{v_1 - v_{out}}{R_f}$$

KCL:

$$i_- = 0 \Rightarrow i_1 = i_2$$

$$\Rightarrow \frac{v_{in} - \left(-\frac{v_{out}}{A}\right)}{R_i} = \frac{\left(-\frac{v_{out}}{A}\right) - v_{out}}{R_f}$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = -\frac{R_f}{R_i} \frac{1}{\frac{R_i + R_f}{AR_i} + 1} \approx -\frac{R_f}{R_i}$$

Transfer Function

$\ll 1 \Rightarrow$  negligible even if  $A \sim 10000$   
 $\therefore A \rightarrow \infty$  is a good approximation

## Important Observations:

- No current flows into the op-amp, i.e.,  $i_-$  and  $i_+ = 0$
- If  $A$  is large and  $v_{out}$  is finite  
 $\Rightarrow v_{id} \approx 0 \Rightarrow v_+ \approx v_-$   
 $\Rightarrow$  Virtual short
- Analysis is only applicable to closed-loop with  $-ve$  feedback

Real Wire

$$V_A \bullet \text{---} \bullet V_B \Rightarrow V_A = V_B \text{ (Real short)}$$

$$V_C \bullet \quad \bullet V_D \Rightarrow V_C \approx V_D \text{ (Virtual short)}$$

# Op-amp Golden Rules


- Rule 1: In a closed loop with –ve feedback, the output attempts to do whatever is necessary to make the voltage difference between the inputs zero

- The voltage gain of a real op-amp is so high that a fraction of a mV difference between the  $V_+$  &  $V_-$  inputs will achieve the desired finite output


- “Virtual short”, i.e.,  $V_+ \approx V_-$

- Rule 2: The inputs draw no current

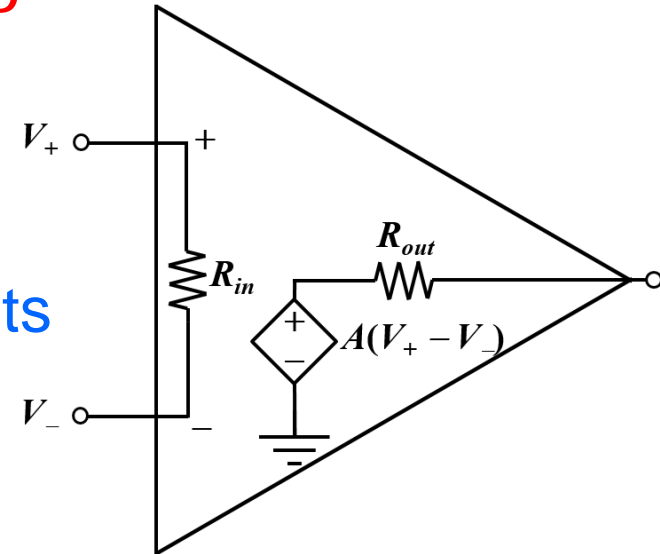
- The ideal op-amp has very large input impedance ( $R_{in}$ ). Thus, the current drawn at the two input terminals  $\sim 0$ .



# What is Closed Loop with –ve Feedback?

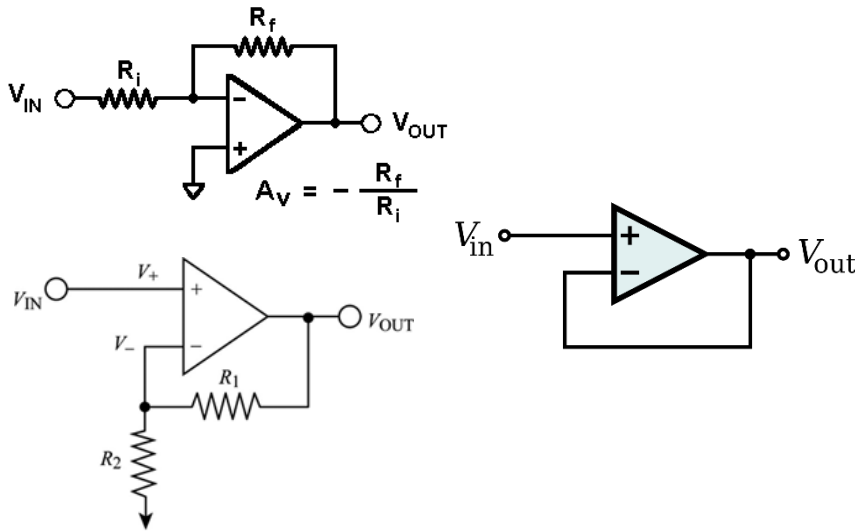


Negative Feedback

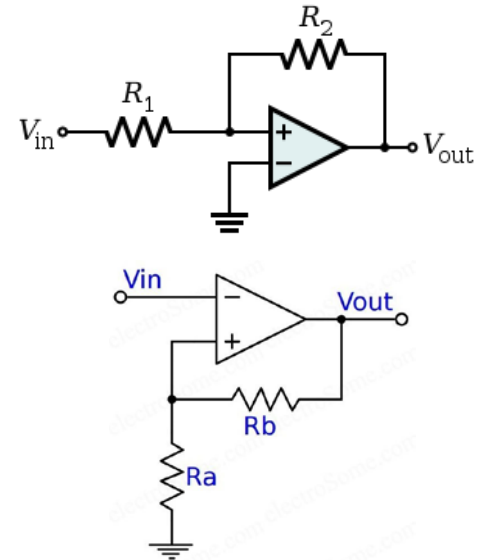

Positive Feedback

- Closed loop: There is connection between output and input
- -ve feedback: The output is fed back to the input in such a way to **reduce** the **output fluctuations**

# Inverting Amplifier

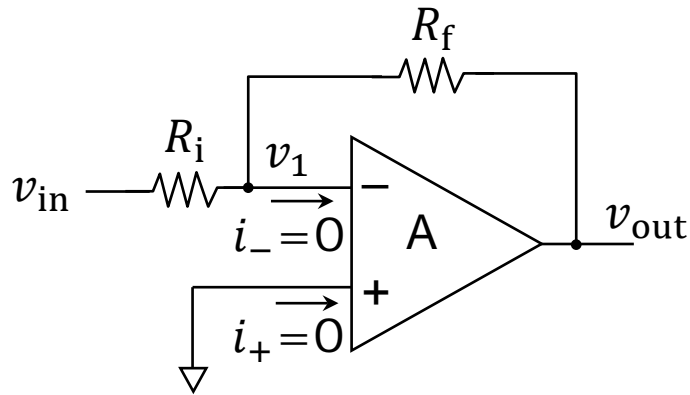

$$\frac{v_{\text{out}}}{v_{\text{in}}} = -\frac{R_f}{R_i}$$


## Derivation based on Golden Rules

$$v_1 = v_- \approx v_+ = 0 \quad [\because \text{Virtual Short}]$$

$$\frac{v_{\text{in}} - v_1}{R_i} = \frac{v_1 - v_{\text{out}}}{R_f} \quad [\because i_- \approx 0]$$

$$\Rightarrow \frac{v_{\text{in}}}{R_i} = \frac{-v_{\text{out}}}{R_f} \Rightarrow \frac{v_{\text{out}}}{v_{\text{in}}} = -\frac{R_f}{R_i}$$

# Non-Inverting Amplifier

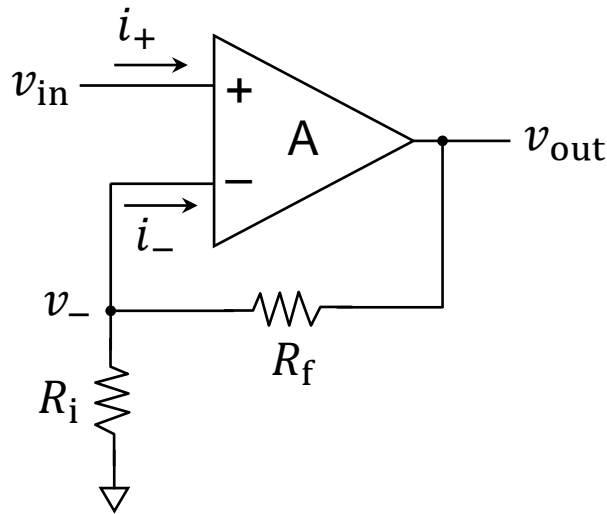

$$\frac{v_{out}}{v_{in}} = 1 + \frac{R_f}{R_i}$$


## Derivation based on Golden Rules

$$v_- \approx v_+ = v_{in} \quad [\because \text{Virtual Short}]$$

$$v_- = v_{out} \times \frac{R_i}{R_i + R_f} \approx v_{in} \quad [\because i_- \approx 0]$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = \left( 1 + \frac{R_f}{R_i} \right)$$

# Significance of Ratio

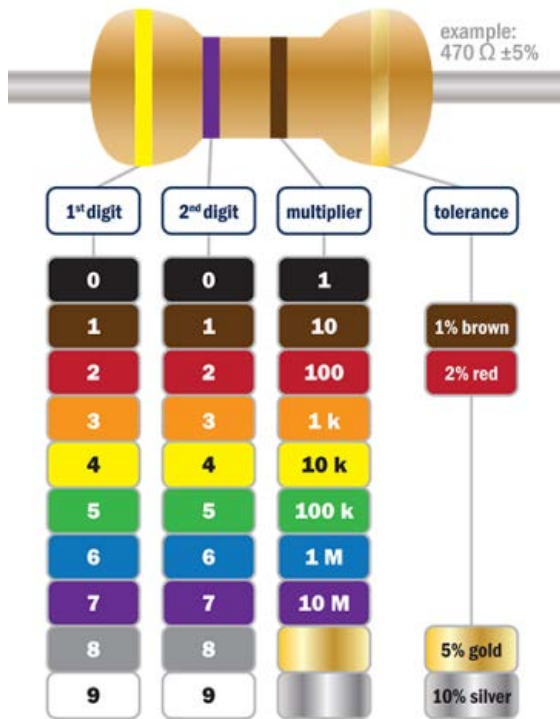

$$\frac{v_{\text{out}}}{v_{\text{in}}} = -\frac{R_f}{R_i}$$

If  $R_f$  and  $R_i$  varies by 5% each, the resulting gain could vary by as much as 10% from desired value!

How to overcome the above issue?

Use resistors from **same batch** (match very well)! For example, if the desired  $R_f/R_i$  ratio is 4, we use 5 identical resistors:  $R_f$  uses 4 resistors, and  $R_i$  uses 1 resistor. An accurate gain of 4 can be obtained!

⇒ Principle exploited in IC design

- Inverting and non-inverting amplifiers are also called **feedback amplifiers**
- One key characteristic is their **gain dependency** on **resistance ratio**
- This is desirable as accurate gain can be obtained despite **component tolerance** and **temperature drift**

# Independent of Temperature Drift

$$R = R_{\text{ref}} [1 + \alpha(T - T_{\text{ref}})]$$

Where,

**R** = Conductor resistance at temperature “T”

**R<sub>ref</sub>** = Conductor resistance at reference temperature **T<sub>ref</sub>**, usually 20°C, but sometimes 0°C.

**α** = Temperature coefficient of resistance for conductor material.

**T** = Conductor temperature in degrees Celcius.

**T<sub>ref</sub>** = Reference temperature that α is specified at for the conductor material

$$\frac{v_{\text{out}}}{v_{\text{in}}} = - \frac{R_{f0} [1 + \alpha(T - T_{\text{ref}})]}{R_{i0} [1 + \alpha(T - T_{\text{ref}})]} = - \frac{R_{f0}}{R_{i0}}$$






Resistors exhibit temperature variation. If resistor of same type with identical temperature coefficients are used, the resulting gain would not drift with temperature.

# Significance of Feedback

Repeater to  
restore signal

Slight signal  
distortion






Repeater to  
restore signal

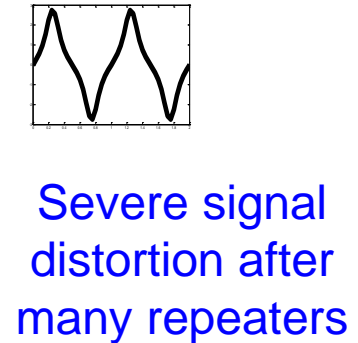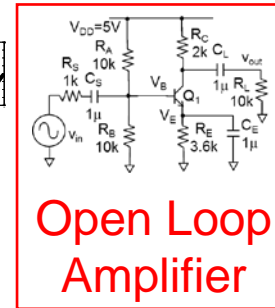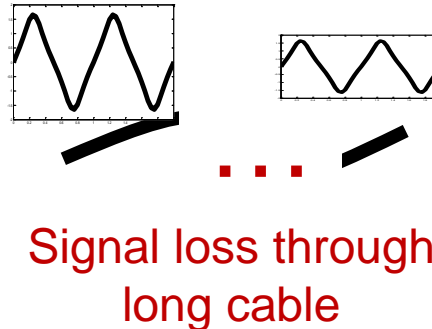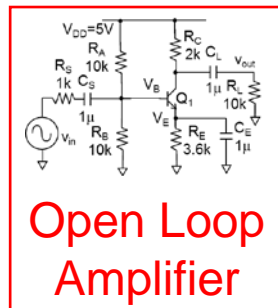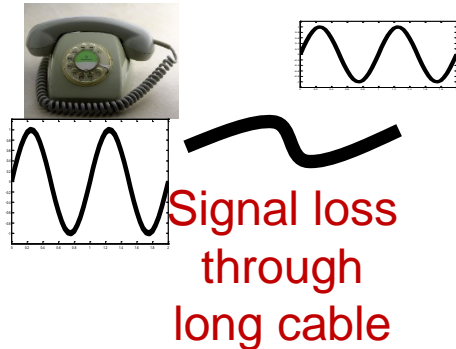

Repeater to  
restore signal

No  
distortion


Repeater to  
restore signal

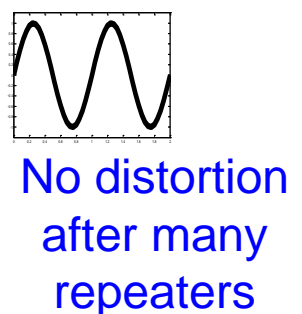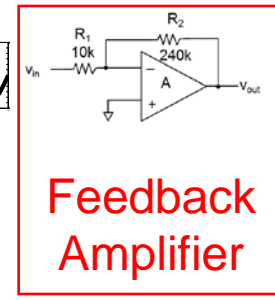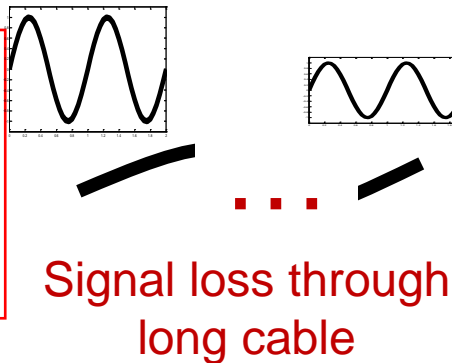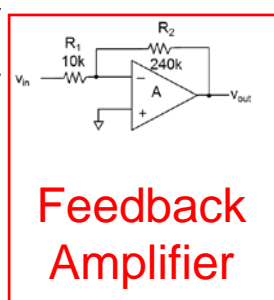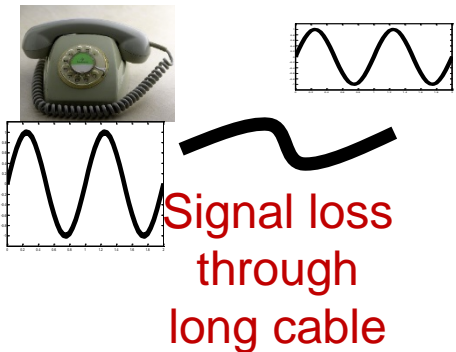

- Harold Stephen Black invented negative feedback amplifier in 1928




# Permissible Resistor Range

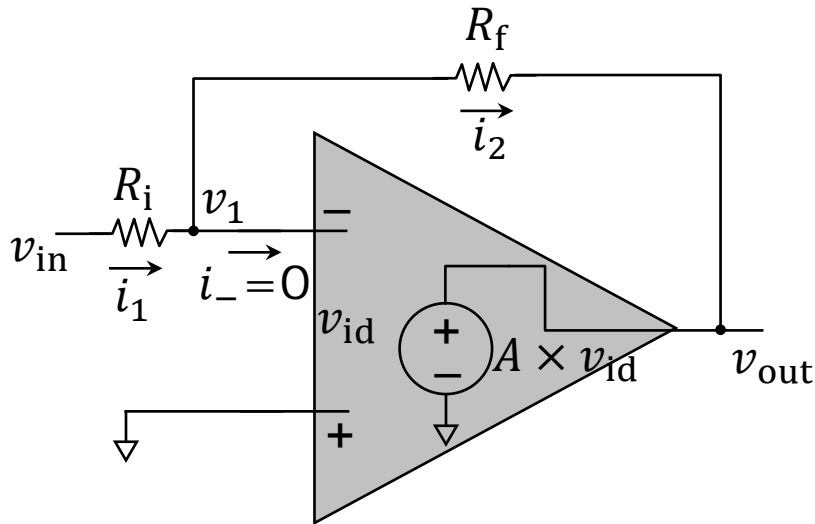

Ideal


VS.

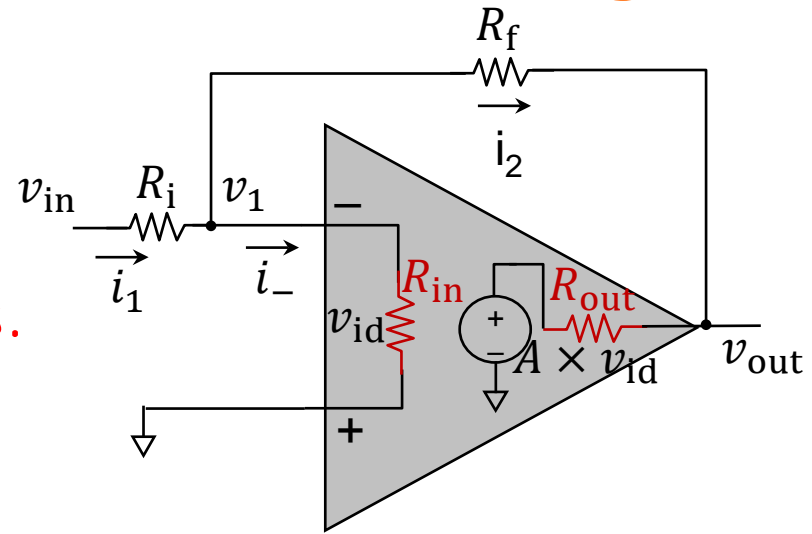


Reality

- In practice,  $i_- \ll i_1$ , and we can **assume**  $i_- \approx 0$
- However, if  $R_i$  is **comparable to**  $R_{in}$ , the current  $i_- = \frac{v_1}{R_{in}}$  would be **comparable to**  $i_1 = \frac{v_{in}-v_1}{R_i}$  (and  $v_{in}$  could be comparable to  $v_1$ ) and we **cannot assume**  $i_- \approx 0$  in our analysis
- Also, if  $R_f$  is comparable to  $R_{out}$ ,  $v_{out}$  would not be equal to  $A v_{id}$
- Hence,  $R_i$  and  $R_f$  must be chosen to be  $\gg R_{out}$ , and  $\ll R_{in}$
- Rule of thumb:  $R_i$  and  $R_f$  should be within  $(10 \times R_{out}, 0.1 \times R_{in})$

# Positive vs Negative Gain

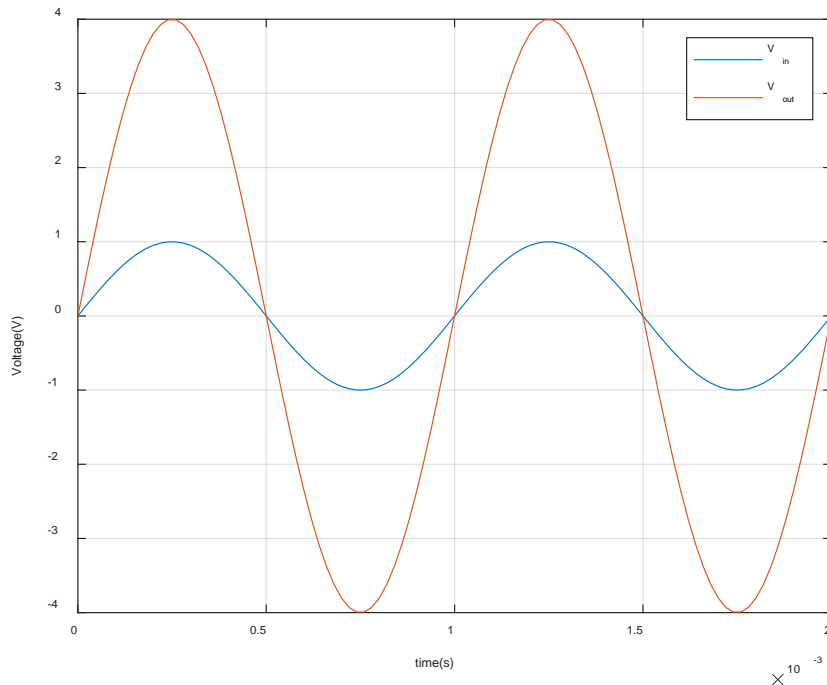

Gain of +4

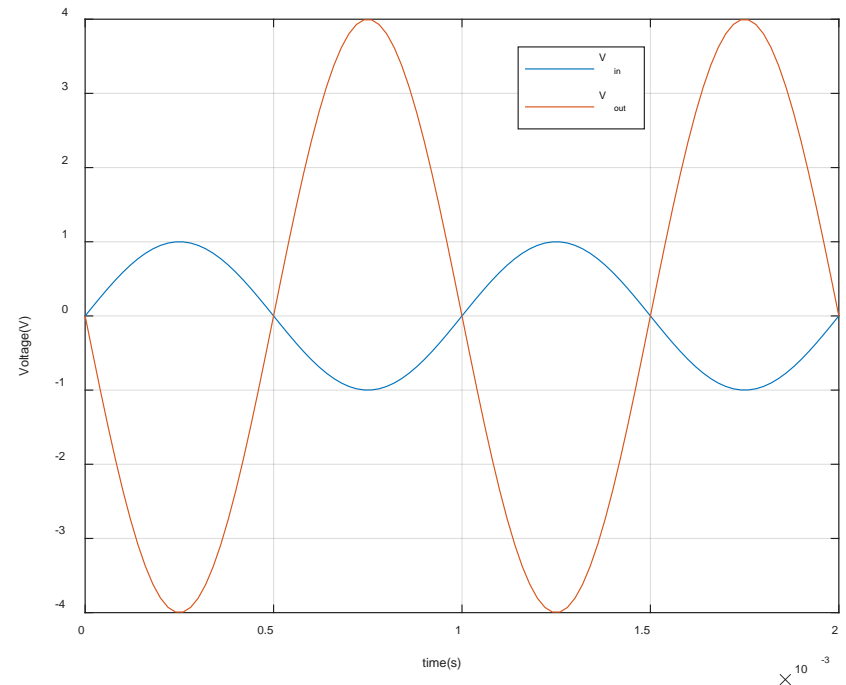


Gain of -4

- **Negative** gain **does not mean loss**
- Negative gain only means output is the **inverted version** of input (180° phase shift)
- Only when gain magnitude is **less than 1**, there is **loss**

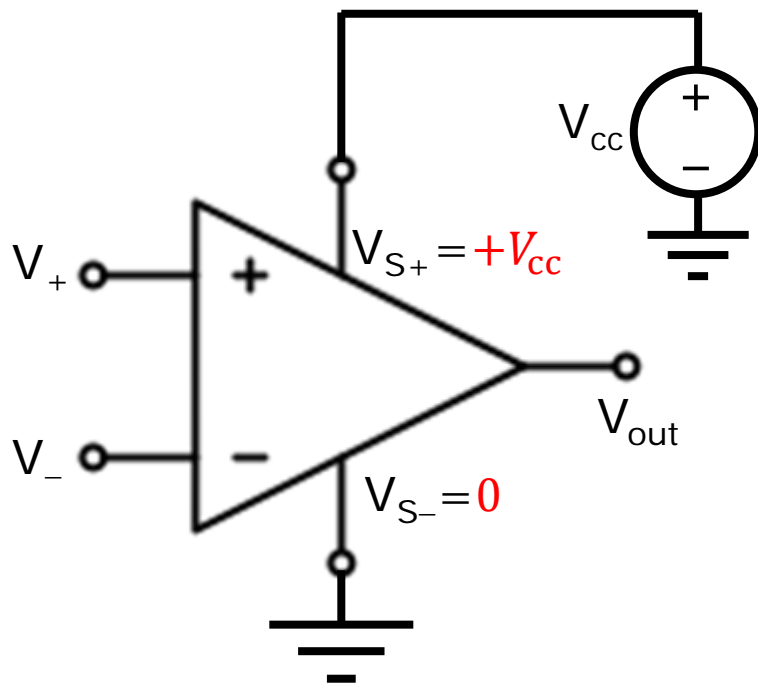
# Single Supply Vs Dual Supply

- An op-amp can be powered either by a **Single** Power Supply or a **Dual** Power Supply



Single Power Supply
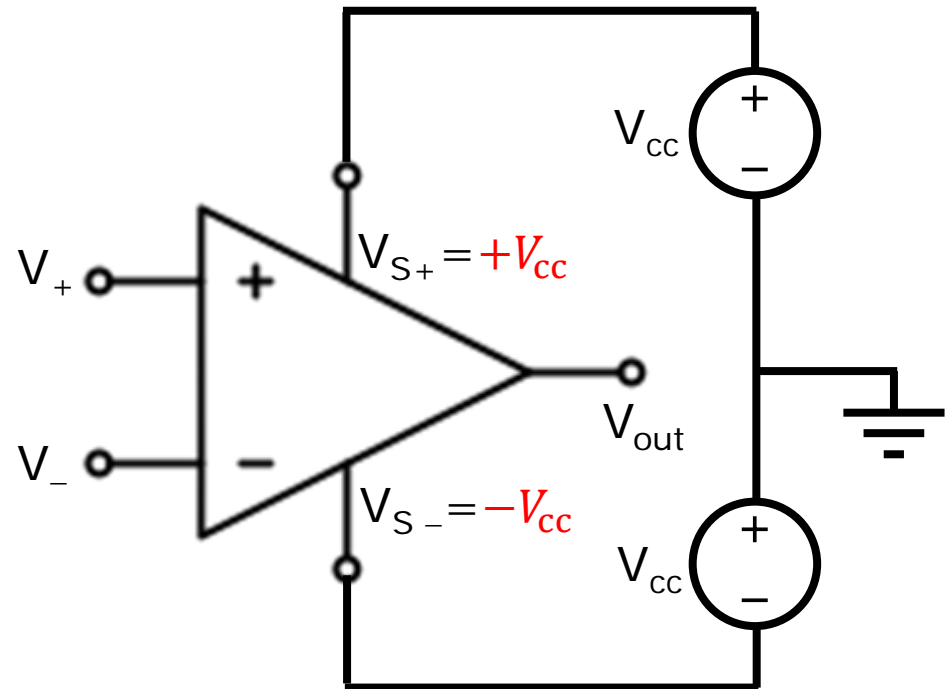
$$(V_{cc} > V_{cc} - V_{ovh} \geq V_{out} \geq V_{ovh})$$



Dual Power Supply

$$(V_{cc} > V_{cc} - V_{ovh} \geq V_{out} \geq -V_{cc} + V_{ovh} > -V_{cc})$$

**THANK YOU**