

MA2011-W2 Dynamical Systems

```
clear all, disp(date)
```

13-Mar-2023

Zero-Order Systems

Here, by zero-order systems, we mean systems for which the output $y(t)$ at any given time t only depends on the current value of the input $x(t)$ but not on its history. These systems can be simply modeled by a, possibly nonlinear, *algebraic equation*, e.g.

$$y(t) = f(x(t), t)$$

The function $f(\cdot, t)$ might or might not depend explicitly on time t , in which case we denote the systems as *time-invariant*:

$$y(t) = f(x(t))$$

The simplest case is that of linear systems, i.e. those which can be simply described by a *linear equation*

$$y(t) = a(t) \cdot x(t) + b(t)$$

The easiest case is when the system is *Linear and Time-Invariant (LTI)*:

$$y(t) = a \cdot x(t) + b$$

i.e. when a and b are constant.

First-Order Systems (LTI) systems

Very often, the output of a system will depend also on the history of the input. Many systems of interest can be described via *Ordinary Differential Equations (ODE)*. Besides its current input $u(t)$, the *state of the system* $x(t)$ will also depend on its time derivatives $\frac{d}{dt}x(t)$, $\frac{d^2}{dt^2}x(t)$, \dots , $\frac{d^n}{dt^n}x(t)$, up to the n -th order.

First-order systems only involve derivatives up the first order, i.e. it will only contain $\frac{d}{dt}x(t)$ (denoted as $\dot{x}(t)$, for short).

A *linear, time-invariant first-order system* can in general be described as

$$\begin{aligned}\dot{x}(t) + \frac{x(t)}{\tau} &= u(t) \\ x(0) &= x_0\end{aligned}$$

where

- τ is the time constant;
- $u(t)$ is the forcing input;

- x_0 is the initial condition.

In MATLAB, this can be easily written as

```
syms x(t) u(t)
syms tau x0 real
assume (tau > 0)           %% NOTE this assumption
myEQ = diff(x) == -x/tau + u  %% first order ODE
```

myEQ(t) =

$$\frac{\partial}{\partial t} x(t) = u(t) - \frac{x(t)}{\tau}$$

myIC = x(0) == x0

myIC = x(0) = x0

dsolve(myEQ, myIC)

ans =

$$e^{-\frac{t}{\tau}} \left(x_0 + \int_0^t e^{y/\tau} u(y) dy \right)$$

A few words on Dynamical Analogies - the heart of mechatronics

 


FIG. 2.1. Graphical representation of the three basic elements in electrical, mechanical rectilinear, mechanical rotational and acoustical systems.

r_E = electrical resistance	r_A = acoustical resistance	r_M = mechanical rectilinear resistance	r_R = mechanical rotational resistance
L = inductance	M = inertance	m = mass	I = moment of inertia
C_E = electrical capacitance	C_A = acoustical capacitance	C_M = compliance	C_R = rotational compliance

figure from [Olson 1958]

- Olson, H. F. (1958). *Dynamical analogies* (Vol. 2729). Princeton: Van Nostrand.

	electrical	mechanical (lin.)	mechanical (rot.)
flow	current [A]: i	lin. vel. [m/s]: \dot{x}	ang. vel [rad/s]: $\dot{\theta}$
effort	voltage [V]: Δv	force [N]: f	torque [Nm]: τ
power [W]	$\Delta v \cdot i$	$f \cdot \dot{x}$	$\tau \cdot \dot{\theta}$
energy [J]	$\int \Delta v \cdot i dt$	$\int f \cdot \dot{x} dt$	$\int \tau \cdot \dot{\theta} dt$
Elements			
resistance	$\Delta v = R i$	$f = b \dot{x}$	$\tau = \beta \dot{\theta}$
inertia	$\Delta v = L \frac{di}{dt}$	$f = m \ddot{x}$	$\tau = I \ddot{\theta}$
compliance	$\Delta v = \frac{1}{C} \int i dt \equiv \frac{q}{C}$	$f = \int k \dot{x} dt \equiv k x$	$\tau = \int \kappa \dot{\theta} dt \equiv \kappa \theta$
En. storage			
kinetic energy	$E = \frac{1}{2} L i^2$	$E = \frac{1}{2} m \dot{x}^2$	$E = \frac{1}{2} I \dot{\theta}^2$
potential energy	$E = \frac{1}{2} C \Delta v^2$	$E = \frac{1}{2} k \Delta x^2$	$E = \frac{1}{2} \kappa \Delta \theta^2$

DC Analysis (response to constant inputs)

Very often, a system is subjected to a constant input

$$\dot{x}(t) + \frac{x(t)}{\tau} = u_0$$

$$x(0) = x_0$$

```
syms u0 real
```

```
myEQ0 = subs(myEQ, u(t), u0)
```

```
myEQ0(t) =
```

$$\frac{\partial}{\partial t} x(t) = u_0 - \frac{x(t)}{\tau}$$

```
DC_Sol = dsolve(myEQ0, myIC)
```

```
DC_Sol =
```

$$\tau u_0 + e^{-\frac{t}{\tau}} (x_0 - \tau u_0)$$

Let's see what happens when $t \rightarrow \infty$, let's define

$$x_\infty := \lim_{t \rightarrow \infty} x(t)$$

```
limit(DC_Sol, t, inf)
```

```
ans = \tau u_0
```

From this, we shall rewrite the first order equation as

$$\dot{x}(t) = \frac{x_\infty - x(t)}{\tau}$$

$$x(0) = x_0$$

```
syms x_inf real
myEQ0 = subs(myEQ, u(t), x_inf/tau)
```

```
myEQ0(t) =
```

$$\frac{\partial}{\partial t} x(t) = \frac{x_{\text{inf}}}{\tau} - \frac{x(t)}{\tau}$$

```
dsolve(myEQ0, myIC)
```

```
ans =
```

$$x_{\text{inf}} + e^{-\frac{t}{\tau}} (x_0 - x_{\text{inf}})$$

and we wish to know how it will respond. In this case, rather than a generic forcing input, we should consider a constant input $u(t)$ and a system initially in its *zero* state, i.e. $x(0) = 0$

```
mylegend = {};
for tau_list = [0.1 0.2 1 2 5 10]
    SOL = dsolve (subs(myEQ0, {x_inf, tau}, {5, tau_list}), 'x(0)==0')
    fplot(SOL, [0 10]); grid on; hold on
    mylegend= {mylegend{:}, ['\tau = ' num2str(tau_list) ' sec']};
    xlabel('time [sec]'); ylabel('x(t) [V]')
    title('x_\infty = 5V')
end
```

$$SOL = 5 - 5 e^{-10 t}$$

$$SOL = 5 - 5 e^{-5 t}$$

$$SOL = 5 - 5 e^{-t}$$

```
SOL =
```

$$5 - 5 e^{-\frac{t}{2}}$$


```
SOL =
```

$$5 - 5e^{-\frac{t}{5}}$$

SOL =

$$5 - 5e^{-\frac{t}{10}}$$

```
legend(mylegend);
```

 

To manually sketch exponential responses given x_0, x_∞, τ it is useful to evaluate the time derivative of the exponential at time $t = 0$, i.e.

$$\dot{x}(0) = \frac{x_\infty - x_0}{\tau}$$

```
subs(myEQ0, t, 0)
```

ans(t) =

$$\left(\left(\frac{\partial}{\partial t} x(t) \right) \right) \Big|_{t=0} = \frac{x_{\text{inf}}}{\tau} - \frac{x(0)}{\tau}$$

as this provides the slope of the tangent line

```
tau_val = 2;
x_0_val = 3;
x_inf_val = 7;
range = [0 3*tau_val];
```

```
MyExp = subs( dsolve(myEQ0, 'x(0)==x0'), {x0, x_inf, tau}, {3, 7, tau_val})
```


```
MyExp =
```

$$7 - 4e^{-\frac{t}{2}}$$

```
MyTaylor = taylor (MyExp, t, 'Order', 2)
```

```
MyTaylor = 2t + 3
```
 
```
figure
fplot(MyExp, range); grid on, hold on
fplot(MyTaylor, range)
fplot(x_inf_val, 'k', range)
fplot(x_0_val, 'k', range)
ylim([x_0_val-2 x_inf_val+2])
title(['\tau = ' num2str(tau_val) ' s'])
legend(char(MyExp), char(MyTaylor), 'x_\infty', 'Location', 'NorthWest')
xlabel('time [sec]'); ylabel('x(t)')
```



AC Steady-State analysis (steady-state response to sinusoidal inputs)

AC-analysis is based on the fact that given a purely sinusoidal input, e.g. $\cos(\omega t)$, after a long time, we expect to see a purely sinusoidal output, e.g. $A_\omega \cos(\omega t + \phi_\omega)$

- at the same frequency ω

- but with likely different (frequency-dependent) Amplitude A_ω and phase ϕ_ω


$$\cos(\omega t) \Rightarrow \|system\| \Rightarrow A_\omega \cos(\omega t + \phi_\omega)$$

The **objective of AC analysis** is to determine Amplitude A_ω and phase ϕ_ω for every input frequency ω

This can be accomplished in basically two ways

- via trigonometric manipulation (hard way)
- via complex exponentials (easy way)

 Let's look at a simple case, a 1st order RC circuit



The hard way - via trigonometry

```
C = 1e-3;           %% F
R = 1e3;            %% Ohms
syms phi t omega real
syms A positive     %% if we don't impose a positive value, we will get two solutions later on
V_in = cos(omega * t)
```

$$V_{in} = \cos(\omega t)$$

$$V_{out} = A * \cos(\omega t + \phi)$$

$$V_{out} = A \cos(\phi + \omega t)$$

Define device equations

```
i = C* diff(V_out)  %% the command 'diff' takes the time derivative
```

$$i = -\frac{A \omega \sin(\phi + \omega t)}{1000}$$

$$V_R = R * i$$

$$V_R = -A \omega \sin(\phi + \omega t)$$

Solve equations $\forall t$, in fact, only for a couple of values, then we can verify that solutions are valid at all times.

$$\text{KVL} = V_{\text{in}} == V_R + V_{\text{out}}$$

$$\text{KVL} = \cos(\omega t) = A \cos(\phi + \omega t) - A \omega \sin(\phi + \omega t)$$

expand (KVL)

$$\text{ans} = \cos(\omega t) = A \cos(\omega t) \cos(\phi) - A \sin(\omega t) \sin(\phi) - A \omega \cos(\omega t) \sin(\phi) - A \omega \sin(\omega t) \cos(\phi)$$

$$\text{myEquations} = [\text{subs}(\text{KVL}, t, 0); \text{expand}(\text{subs}(\text{KVL}, t, 1/\omega \pi/2))]$$

myEquations =

$$\begin{pmatrix} 1 = A \cos(\phi) - A \omega \sin(\phi) \\ 0 = -A \sin(\phi) - A \omega \cos(\phi) \end{pmatrix}$$

$$\text{myVariables} = [A; \phi]$$

myVariables =

$$\begin{pmatrix} A \\ \phi \end{pmatrix}$$

$$\text{SOL} = \text{solve}(\text{myEquations}, \text{myVariables})$$

SOL = struct with fields:

$$\begin{array}{l} A: [1 \times 1 \text{ sym}] \\ \phi: [1 \times 1 \text{ sym}] \end{array}$$

$$\text{SOL.A}, \text{SOL.}\phi$$

ans =

$$\frac{1}{\sqrt{\omega^2 + 1}}$$

ans =

$$-2 \operatorname{atan}\left(\frac{\sqrt{\omega^2 + 1} - 1}{\omega}\right)$$

NOTE: that $-2 \tan^{-1}\left(\frac{\sqrt{\omega^2 + 1} - 1}{\omega}\right) \equiv -\tan^{-1} \omega$

However, this is a very cumbersome (too much trigonometry) way to proceed!!!

The easy way via the 'complex trick'

again, start from the the time-domain equations, for simplicity let's set $\tau = 1$

$$\text{myEQ} = \text{subs}(\text{myEQ}, \tau, 1)$$

myEQ(t) =

$$\frac{\partial}{\partial t} x(t) = u(t) - x(t)$$

Now, let's consider **complex exponentials** as inputs

$$e^{j\omega t} \Rightarrow \left| \begin{smallmatrix} LTI \\ SYS \end{smallmatrix} \right| \Rightarrow A_{\omega} e^{j(\omega t + \phi_{\omega})} = \underbrace{A_{\omega} e^{j\phi}}_{H(j\omega)} e^{j\omega t}$$

```
syms H_0 complex
syms omega real
j=sqrt(-1);
myEQ_AC = subs(myEQ, {u(t), x(t)}, {exp(j*omega *t), H_0 * exp(j*omega *t)})
```

$$\text{myEQ_AC}(t) = H_0 \omega e^{\omega t} i = e^{\omega t} i - H_0 e^{\omega t} i$$

```
eqn_cmplx = simplify(myEQ_AC)
```

$$\text{eqn_cmplx}(t) = H_0 (1 + \omega i) = 1$$

```
% simplify (real(AC_Sol_complex) - AC_Sol)
Sol_myEQ_AC = solve(eqn_cmplx, H_0)
```

```
Sol_myEQ_AC =
```

$$\frac{1}{1 + \omega i}$$

Bode Plots

```
freq = logspace(-2, 2, 100);
H = subs(Sol_myEQ_AC, { tau, omega}, {1, 2*pi*freq} );
figure
subplot(2,1,1)
loglog(freq, abs(H)); grid on; ylabel('amplitude'); title ('Bode Plots')
hold on
subplot(2,1,2)
semilogx(freq, angle(H)); grid on; xlabel('frequency [Hz]'); ylabel('phase [rad]')
hold on
```

Cut-off frequency: the frequency at which the output is reduced by -3dB (or $1/\sqrt{2}$), clearly for a first order system

```
omega_0 = subs(1/tau, tau, 1)
```

```
omega_0 = 1
```

```
f_0 = omega_0/2/pi
```

```
f_0 =
```


$$\frac{1}{2\pi}$$

```
H_0 = subs(Sol_myEQ_AC, {tau, omega}, {1, 1} );
```

```

subplot(2,1,1)
loglog(omega_0/2/pi, abs(H_0) , 'ro')
subplot(2,1,2)
semilogx(omega_0/2/pi, angle(H_0) , 'ro')


```

 

2nd order dynamics

Newton's law

Consider a mass-spring-damper case:

 


```
syms m b k real
syms f(t) x(t)
eqn_Newton = f(t) == m*diff(x(t), 2)+b*diff(x(t)) + k*x(t)
```

```
eqn_Newton =
```

$$f(t) = m \frac{\partial^2}{\partial t^2} x(t) + b \frac{\partial}{\partial t} x(t) + k x(t)$$

Time Response to constant forcing Input

```
figure;
mylegend = {};
for b_var = [0.1, 0.5, 1, 5, 10]
    mylegend = {mylegend{:}, ['b = ' num2str(b_var) 'N.s/m']};
    eqn_Newton_DC = subs(eqn_Newton, {f(t), m, b, k}, {1, 1, b_var, 1});
    Dx = diff(x);
    cond = [x(0)==0, Dx(0) == 0];
    Sol_Newton_time = dsolve(eqn_Newton_DC, cond);
    fplot(Sol_Newton_time, [0 20]); grid on; hold on
end
xlabel('time [sec]'); ylabel('x(t)'); title ('constant forcing input f(t)=1')
legend(mylegend)
```

 

AC Analysis

```
syms omega real
syms F_0 X_0 complex
```

```
AC_Exp_Newton = subs(eqn_Newton, {f(t), x(t)}, {F_0*exp(j*omega*t), X_0*exp(j*omega*t)})
```

$$AC_Exp_Newton = F_0 e^{\omega t i} = X_0 k e^{\omega t i} + X_0 b \omega e^{\omega t i} i - X_0 m \omega^2 e^{\omega t i}$$

```
simplify( AC_Exp_Newton )
```

$$ans = X_0 m \omega^2 + F_0 = X_0 (k + b \omega i)$$

```
Sol_ODE2= solve(simplify (AC_Exp_Newton) , X_0)
```

```
Sol_ODE2 =
```

$$\frac{F_0}{-m \omega^2 + i b \omega + k}$$

```
freq = logspace(-2, 1, 100);
H = subs(Sol_ODE2,{F_0, m, b, k, omega}, {1, 1, .1, 1, 2*pi*freq} );
figure
subplot(2,1,1)
loglog(freq, abs(H)); grid on; ylabel('amplitude'); title ('Bode Plots')
subplot(2,1,2)
semilogx(freq, angle(H)); grid on; xlabel('frequency [Hz]'); ylabel('phase [rad]')
```

